




Answer the Following Questions:

Q1

Using the principle of superposition to find I_o and V_o .


10

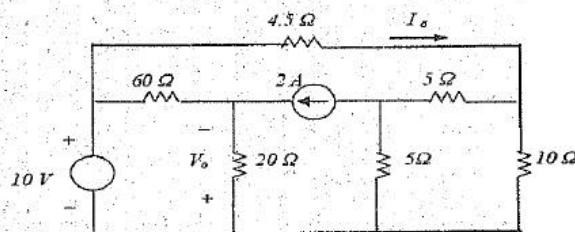

Q2

The laminated sheet steel section in the figure has a stacking factor 0.9. Compute the current required to establish a flux $\phi = 1.4 \times 10^{-4}$ Wb. Neglect fringing. (Take 1"=2.54 cm)


10

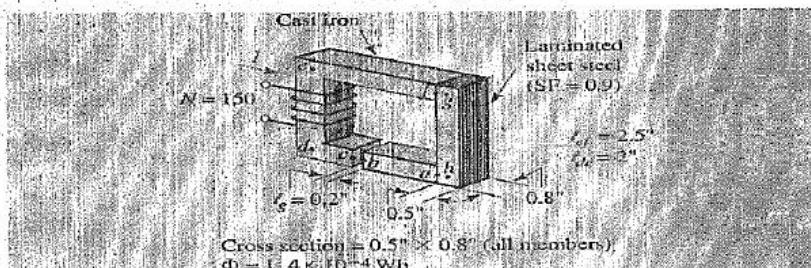

Q3

Find the effective value of the waveform shown in the following figure over one cycle.


10

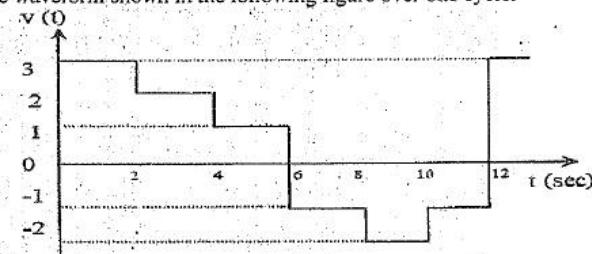


Q4

For the circuit shown below:

$$e(t) = 70.7 \sin 377t$$

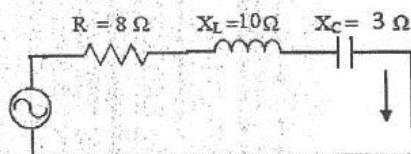

- a- Find the total impedance Z in polar form.
- b- Draw the impedance diagram.
- c- Find the value of C in μF and the value of L in henry.
- d- Find the current I and the voltages V_R , V_L and V_C in polar form.
- e- Draw the phasor diagram of voltages V_R , V_L and V_C and the current I .
- f- Verify Kirchhoff's voltage law around the closed loop.
- g- Find the average power delivered to the circuit.
- h- Find the power factor of the circuit and indicate whether it is leading or lagging.
- i- Find the sinusoidal expressions for the voltages and current.
- j- Plot the waveforms for the voltages and current on the same set of axes.
- k- find the capacitance needed to correct power factor to 0.98 and where its position.

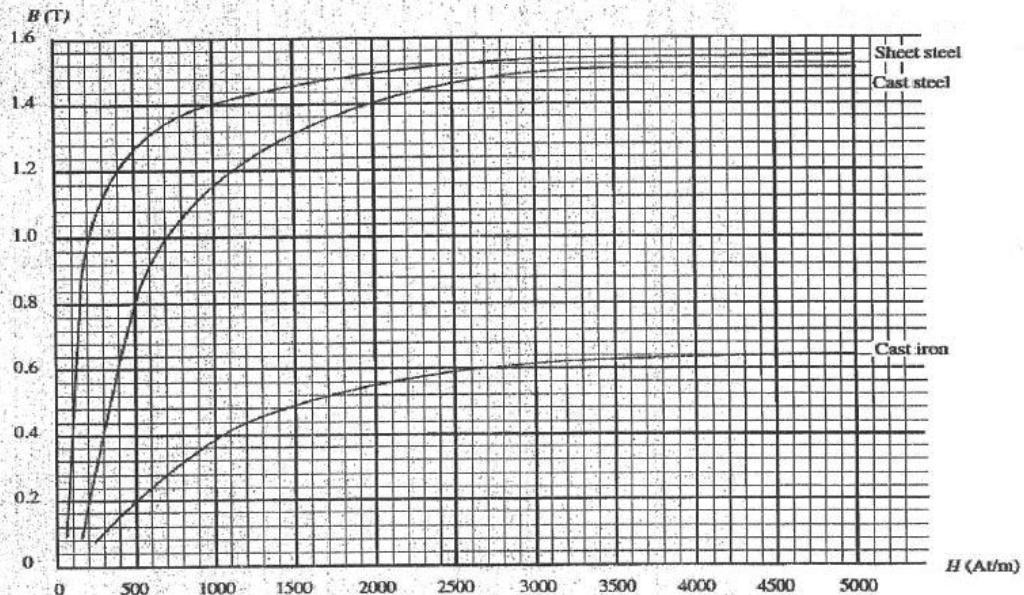

End of Exam Questions, Good Luck
Dr. fathallaselim