

University
 of Engineering
 Department: Electrical Engineering
 Year: 3rd (2007)/2017-2018
 Subject: Electric Tests (2)
 Name: Dr. Amlak Abaza

Date: 14-1-2018 ①
 Time Allowed: 3 hours
 Full Mark: 60
 Final Exam: 2nd Term
 Academic Code: EPM3005

Answer Model

Question 1: (a) The connection diagram to perform
 (i) the load characteristic curve of separately
 excited DC generator

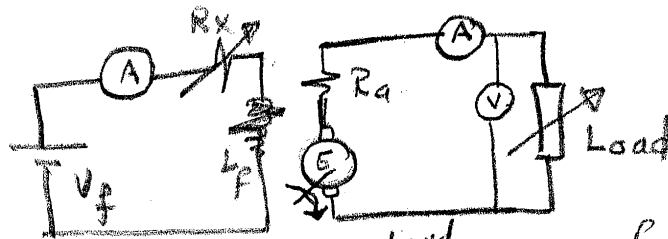


Fig.1: Connection diagram of load characteristic curve of separately excited DC generator

(ii) Load characteristic curve of self-excited
 DC shunt generator.

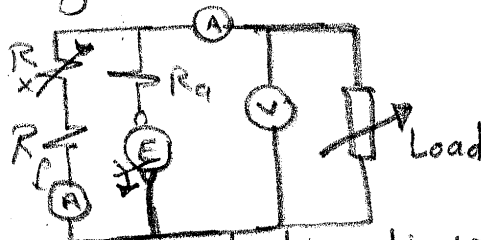


Fig.2: Connection diagram of DC shunt generator

(b) An experiment to perform Load test of separately-excited DC generator

- 1- Connect the circuit as shown in Fig.1 at no load.
- 2- Rotate the prime-mover of the generator at rated speed
- 3- Adjust the field resistance to control the output voltage of the generator.
- 4- After the o/p voltage reaching the rated voltage set the load resistance to maximum value.

record the ammeter and voltmeter (of the external load) reading


- 5- Change the Load resistance to increase the Load current by steps and record the terminal voltage and current (V_L, I_L) at each step.

6- At each step be sure that the speed is at its rated rpm

I_L	—	—					$E_L = E_{rat}$
V_L	—	—					

7- If the speed changed, adjust the field resistance to restore it to its nominal value

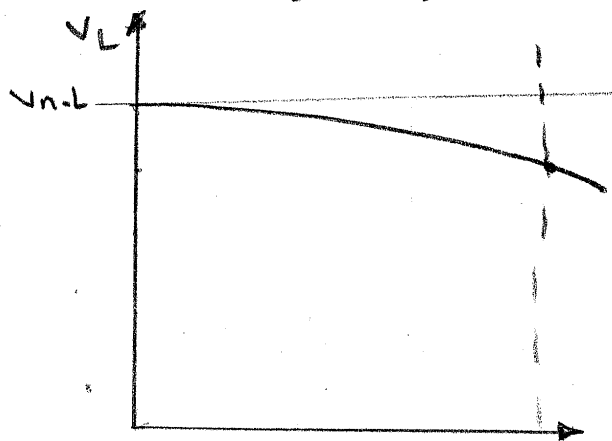8- Draw the external characteristic curve ($V_E - V_L$)



9- Notice the drop in terminal voltage with $I_{L,rat}$ increase the load current

* Interpretation of The Results

It is noticed that $V_L \downarrow$ with $I_L \uparrow$, this is because :

$$V_L = E_a - I_a R_a \quad \left\{ \begin{array}{l} I_L = I_a \\ R_a \text{ is the armature resistance} \end{array} \right.$$

$$\Rightarrow V_L = E_a - I_L R_a$$

$$\therefore E_a = k \phi n = \text{const}$$

\Rightarrow by increasing $I_L \Rightarrow$ decreasing V_L (voltage drop on the R_a)


(C)

The open circuit char curve of separately excited DC generator At 1500 r.p.m

$$E_{a2} = E_{a1} * \frac{I_{f2}}{I_{f1}} * \frac{n_2}{n_1} \Rightarrow E_{a2} = E_{a1} * \frac{1500}{1000} \text{ at the same } I_f$$

$I_f (A)$	0.2	0.4	0.6	0.8	1	1.2	1.4	1.6
$E_a _{n=1000 \text{ r.p.m}}$	30	55	75	90	100	110	115	120
$E_a _{1500 \text{ r.p.m}}$	45	82.5	112.5	135	150	165	172.5	180

(i)

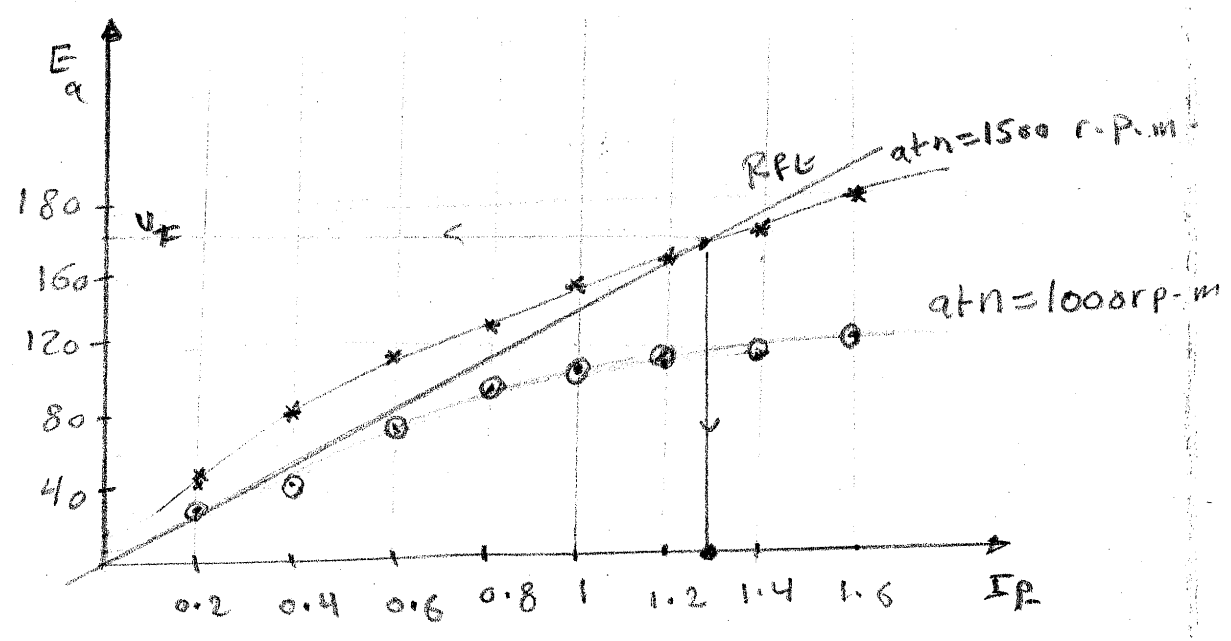

(ii) Yes the generator produces em.f at $I_f = 0.0$ this due to residual magnetism $(B_r)^F$ in the core. and at $n = \text{rated value} \Rightarrow$ small E_a

(iii) $R_{FE} = \frac{V_f}{I_f} = \frac{170}{1.25} = 136 \Omega \therefore R_{FE} = R_f + R_x$
 $\Rightarrow R_x = 130 \Omega$

Q2: (a) Starting test of DC shunt (generator / or motor)


(b) If a DC shunt motor is loaded the speed can be adjusted by the following methods:

- (i) Input voltage
- (ii) Field resistance \rightarrow It is a preferred method because it gives a smooth change in speed.

③. $V_L = 200\text{ V}$, $P = 5\text{ kW}$, $R_a = 0.05\ \Omega$ (operates as shunt motor)

④

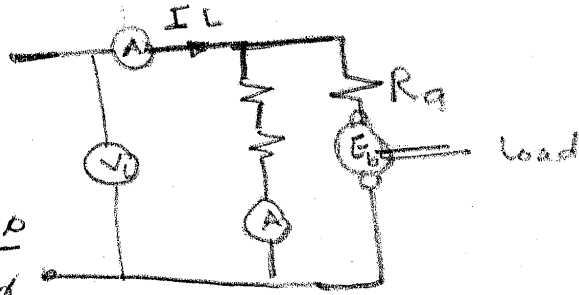To limit I_{Lst} to 110% of full Load current:



$$\therefore I_{Lrat} = \frac{P_{in}}{V_L} = \frac{5000}{200} = 25\text{ A}$$

DC shunt motor

[Assuming % efficiency $\rightarrow P_{in} \neq P_o$]

$$\therefore I_{Lst} = \frac{110}{100} \times 25 = 27.5\text{ A}$$

At starting $n = 0 \Rightarrow E_b = 0$

$$\therefore \frac{V_L}{R_a} = \frac{V_L - E_b}{R_a} \Rightarrow I_{Lst} = \frac{V_L}{R_{at}}$$

\therefore to make I_{Lst} as 27.5 A \rightarrow It must be insert a series resistance with armature limit the starting current \Rightarrow

$$R_{at} = \frac{200}{27.5} = 7.272\ \Omega$$

$$R_{at} = R_a + R_{add}$$




$$R_{add} = R_{at} - R_a = 7.272 - 0.05 = 7.222\ \Omega$$

This method has drawback, as the Power loss on the R_{add}
Another method:

We can start DC shunt motor by adjust the input voltage. At starting (start with small value until the E_b exist and then \rightarrow its rated value)

13:

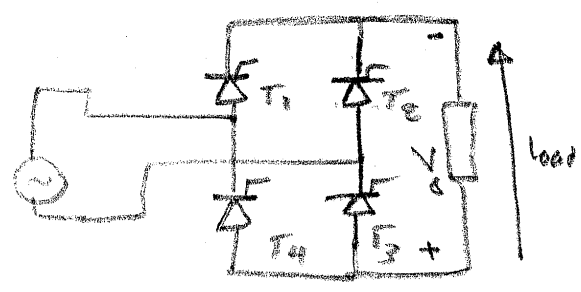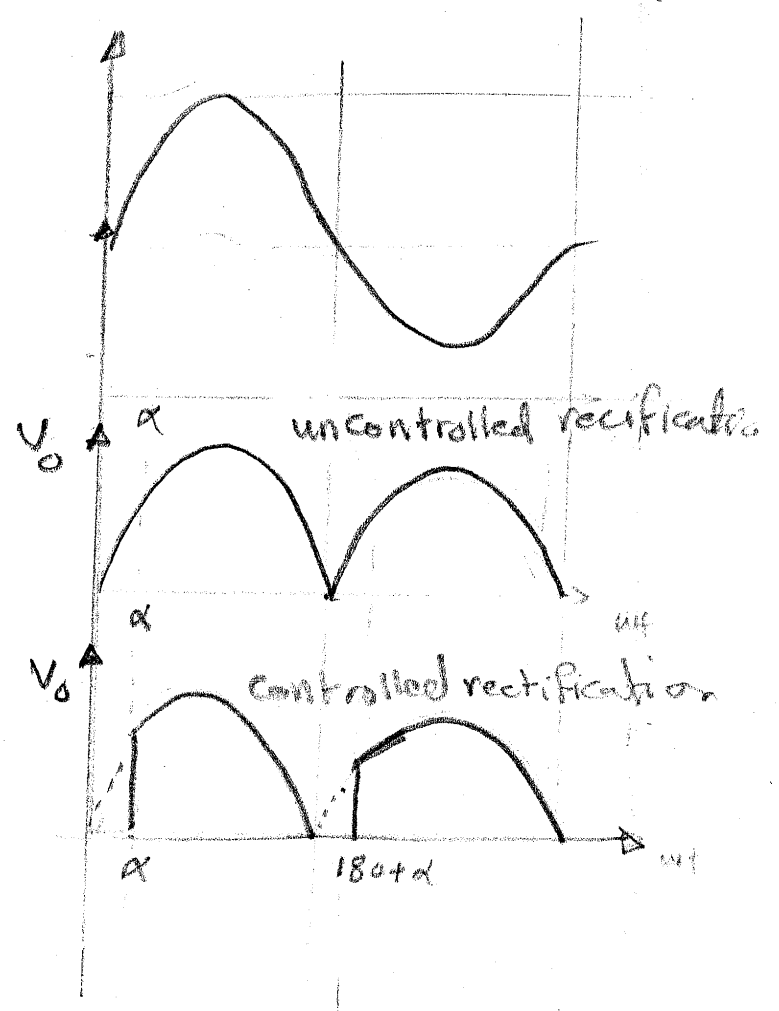
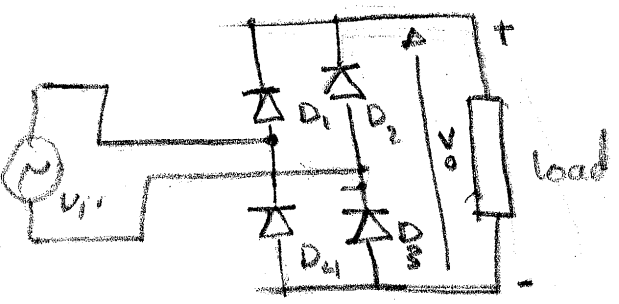
(a) DC source from 1-ph AC (full wave uncontrolled and controlled rectification)




(b) The effect of :

(i) Inductive Load for the rectifier circuit


For half-wave uncontrolled rectifier

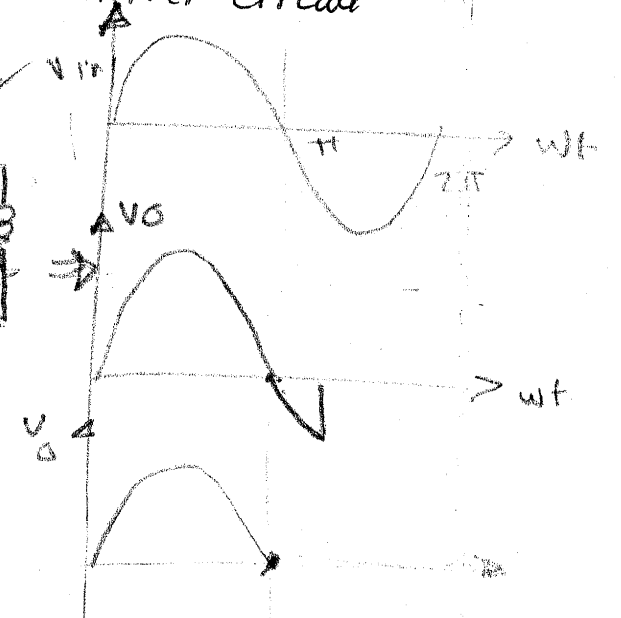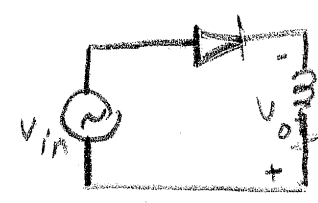

(ii) Freewheeling diode

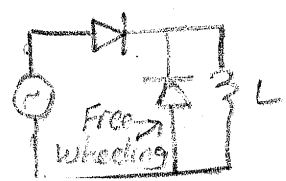

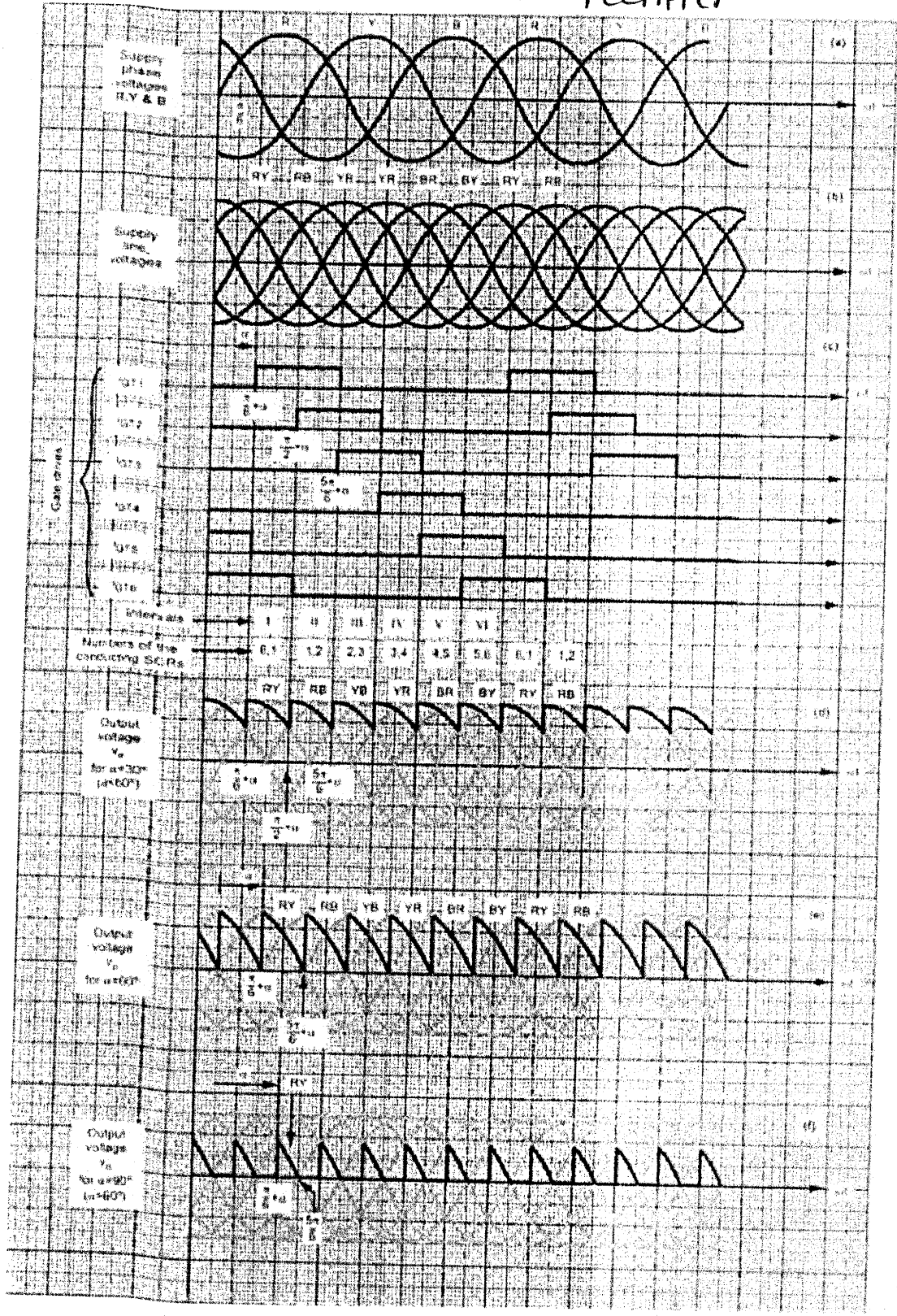Q4: o/p voltage from Three phase full wave controlled rectifier



For $\alpha = 30^\circ$

For $\alpha = 60^\circ$

For $\alpha = 90^\circ$

For $\alpha = 120^\circ$

$V_o = 0 - d$

Fig 4: Waveform of Three Phase Fully Controlled Bridge Rectifier

Φ_4

7

- (b)
- (i) The terminal voltage of self-ex. DC generator
 $V_T = 0$ because
- ① There is no residual magnetism
 - ② reverse connection of armature terminal
- (ii) speed increase with increase R_{xf} (added resistance to field):
DC shunt motor
Because :
- $$n \propto \frac{E_a}{\Phi} \Rightarrow n \propto \frac{V_L - I_a R_a}{K(I_f)}$$
- IF we increase the external field resistance \Rightarrow
decrease the field current, I_f , and then
increase the speed of the motor
- (iii)