
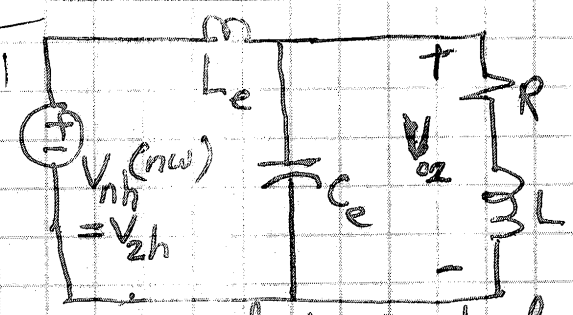


1 25 Marks

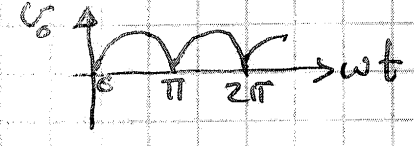$R = 40 \Omega$
 $L = 10 \text{ mH}$, $f = 60 \text{ Hz}$
 $RF = 0.1$
 $L_e = ?$, $C_e = ?$



Equivalent circuit of harmonics



Solution

→ * To avoid passing of n th harmonic ripple through load,

step I $\frac{1}{n\omega C_e} \ll \sqrt{R^2 + (n\omega L)^2}$

step 2 take $10 \times \frac{1}{n\omega C_e} = \sqrt{R^2 + (n\omega L)^2} \Rightarrow \boxed{C_e = 326 \mu\text{F}}$

→ * For the 1- ϕ , full-wave uncontrolled rectifier, the dominant harmonic is the second. So the subscript 2 in the following steps denotes the second harmonic.

step 1 $V_{o,dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi}$


step 2 From Fourier analysis of the waveform, the second harmonic is ^{Voltage}

$V_{2h}(\omega t) = \frac{4V_m}{3\pi} \cos 2\omega t$

$V_{2h,rms} = \frac{4V_m}{3\sqrt{2}\pi}$ ← the source of harmonics

step 3 $V_{o2,rms} = V_{2h,rms} \left| \frac{-1/n\omega C_e}{n\omega L_e - \frac{1}{n\omega C_e}} \right|$ ← (using voltage divider)


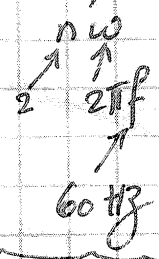
step 4 $RF = 0.1 = \frac{V_{ac}}{V_{dc}} = \frac{V_{o2,rms}}{V_{o,dc}}$
 $= \frac{V_{2h,rms}}{V_{o,dc}} \frac{1}{(4\pi f)^2 L_e C_e - 1} = \frac{\sqrt{2}}{3} \frac{1}{(4\pi f)^2 L_e C_e - 1}$
 $\Rightarrow \boxed{L_e = 30.8 \text{ mH}}$



2

20 Marks


a) $E=0, L=\infty, \alpha=90^\circ$

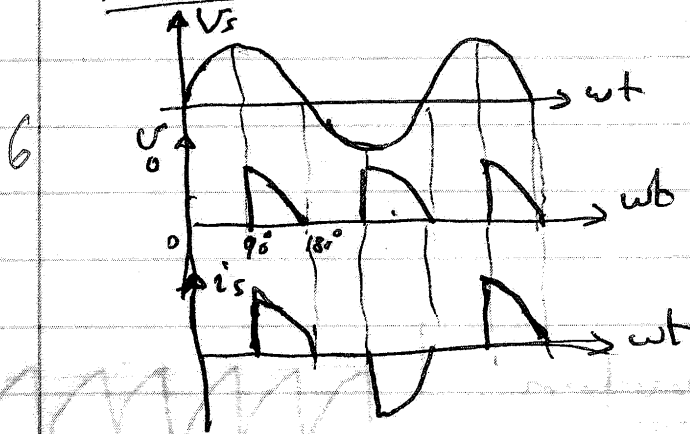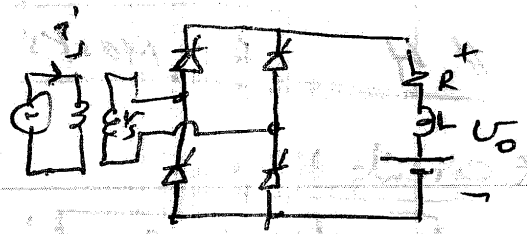

$$U_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{\pi} (\cos \alpha + 1) = \frac{V_m}{\pi}$$

b) $E=0, L=\infty, \alpha=45^\circ$

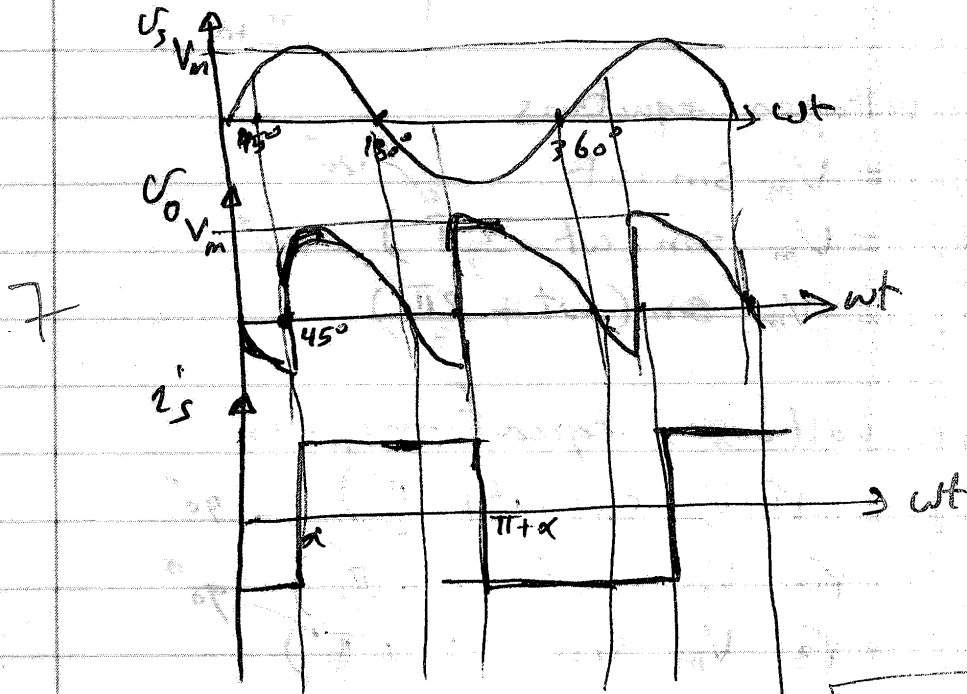



$$U_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d\omega t = \frac{2 V_m \cos \alpha}{\pi} = \frac{\sqrt{2} V_m}{\pi}$$

c) $E=50 \text{ Volt}, L=\infty, \alpha=45^\circ$

same solution as case b).

$$\frac{2 V_m}{\pi} \times \frac{1}{\sqrt{2}} = \frac{\sqrt{2} V_m}{\pi}$$

25 Marks

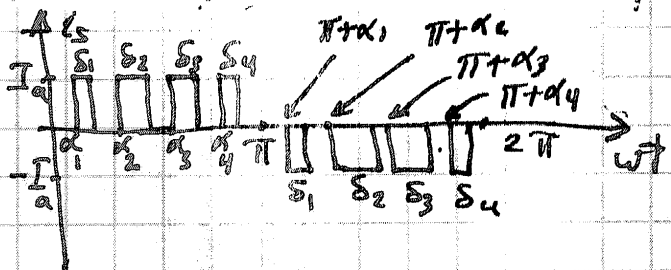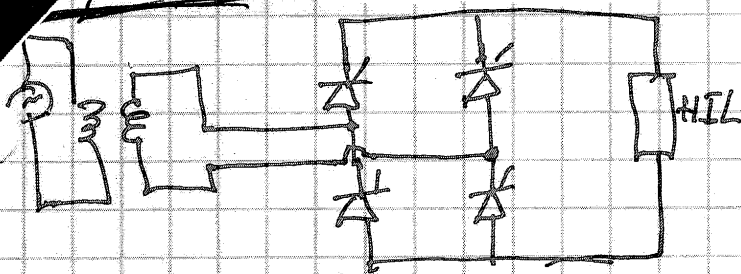

Circuit Diagram

Step 1 Assume values of $\alpha_1, \alpha_2, \alpha_3, \alpha_4, \delta_1, \delta_2, \delta_3, \delta_4$
 (π is, δ is, α is for off, on π is δ is)

Step 2 Due to symmetry of source current waveform (i_s), $I_{dc} = 0$ and $a_n = 0$.

$$b_n = \frac{1}{\pi} \int_0^{2\pi} i_s(t) \sin n\omega t d(\omega t)$$

$$= \frac{1}{\pi} \left[\int_{\alpha_1}^{\alpha_1 + \delta_1} I_a \sin n\omega t d(\omega t) + \int_{\alpha_2}^{\alpha_2 + \delta_2} I_a \sin n\omega t d(\omega t) + \int_{\alpha_3}^{\alpha_3 + \delta_3} I_a \sin n\omega t d(\omega t) \right.$$

$$+ \int_{\alpha_4}^{\alpha_4 + \delta_4} I_a \sin n\omega t d(\omega t) - \int_{\pi + \alpha_1}^{\pi + \alpha_1 + \delta_1} I_a \sin n\omega t d(\omega t) - \int_{\pi + \alpha_2}^{\pi + \alpha_2 + \delta_2} I_a \sin n\omega t d(\omega t)$$


$$\left. - \int_{\pi + \alpha_3}^{\pi + \alpha_3 + \delta_3} I_a \sin n\omega t d(\omega t) - \int_{\pi + \alpha_4}^{\pi + \alpha_4 + \delta_4} I_a \sin n\omega t d(\omega t) \right]$$

Step 3 $i_s(t) = \sum_{n=1,3,5,7,9} b_n \sin n\omega t$
 بعد التوسيع α δ π δ α δ π δ α δ

Step 4 calculate I_{s1} (at $n=1$), I_{s3} , I_{s5} , I_{s7} , I_{s9}

Step 5 Draw spectrum diagram

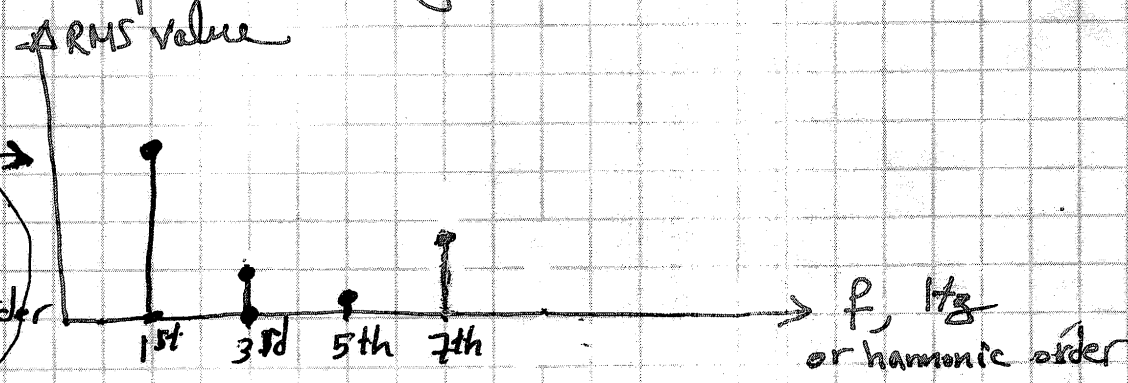1st should be the highest
 - 5th close to zero
 - increase of 4 pulses per π , then rms increases as the harmonic order increasing.




4


20 Marks

(4 Marks for each)

* Circuit diagram 4

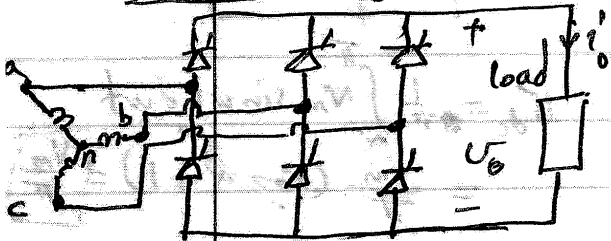

* output voltage waveform 4

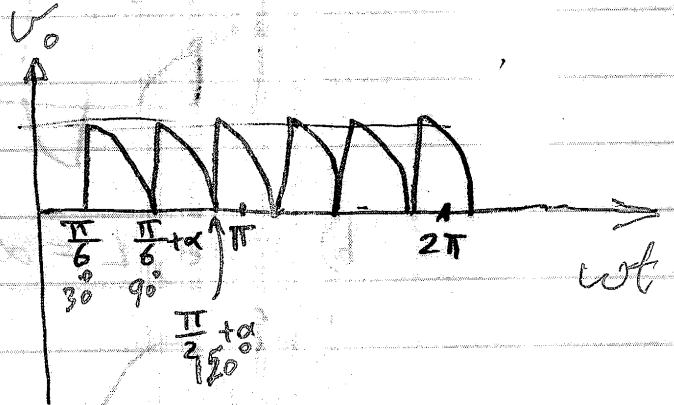

* phase voltages equations 4

$$V_{an} = V_m \sin \omega t$$

$$V_{bn} = V_m \sin \left(\omega t - \frac{2\pi}{3} \right)$$

$$V_{cn} = V_m \sin \left(\omega t + \frac{2\pi}{3} \right)$$

* line voltages equations 30° 4

$$V_{ab} = \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{6} \right)$$

$$V_{bc} = \sqrt{3} V_m \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$V_{ca} = \sqrt{3} V_m \sin \left(\omega t + \frac{5\pi}{6} \right)$$

* Average output voltage $\frac{\pi}{2} + \alpha$ 4

$$V_{dc} = \frac{3}{\pi} \int_{\pi/6 + \alpha}^{\pi/2 + \alpha} V_{ab} d(\omega t) = \frac{3}{\pi} \int_{\pi/6 + \alpha}^{\pi/2 + \alpha} \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{6} \right) d(\omega t)$$

$$= \frac{3\sqrt{3} V_m}{\pi} \cos \alpha$$