


Kafrelsheikh University Faculty of Engineering Electrical Engineering Programme. Department: Electrical Power and Machines Course Title: Elective Course (I). Power System Protection		Date: Sun., 5 - 6- 2016 Time Allowed: 3 hrs Full Mark: 90 Marks Final term Exam: 2 nd Term. Course Code: EPM 3213. Year: 3 rd (2007) / 2015-2016
--	---	---

- Trust in God ----Be confident -----Be calm
- Exam is not a punishment or a curse .
- It is a chance to show your knowledge
- It is the time to get the prize of your effort

Important instructions for all students: please read carefully

- The examination consists of 5 questions in 2 papers (4 pages)
- Read the questions carefully before answering.
- Your answer should be short and precise.
- Remember to mark your answers with ordered numbers corresponding to questions.

Answer the Following Question:

Question (1):

(15 Marks)

a) **Give an account on:** Short transmission line protection challenges and SIR source impedance ratio margin. [6]

b) **Describe** the behavior of protective devices used for distribution system shown in Fig. 1 for different faults at points A, B, C.[9]

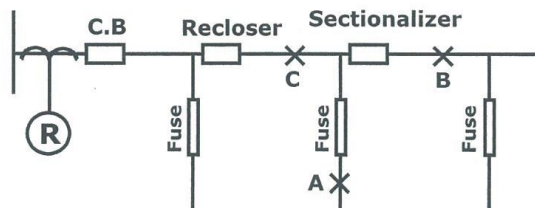


Fig. 1

Question (2):

(20 Marks)

a) **Explain how** to use the directional over-current relay to parallel feeders application shown in Fig. 2. **And how to make** coordination for parallel feeders. Assuming the worst conditions.[8]

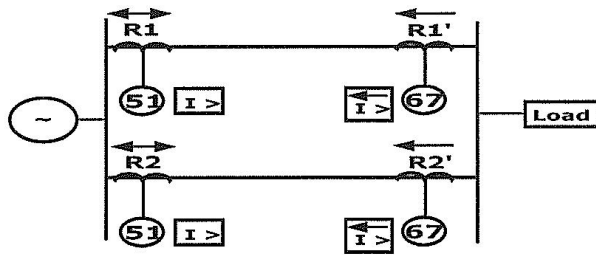


Fig.2

b) Think of yourself as a design protection engineer for the two arrangements of two feeders are in the Fig.3a&3b, which is to be protected by distance relay. Clearly, the continuous current *and voltage rating* of the design will be important, and the maximum fault current that can be interrupted must be determined. *What other features* should be considered in the second zone setting design, if it is to meet the requirements of the distribution protection engineer?[12]

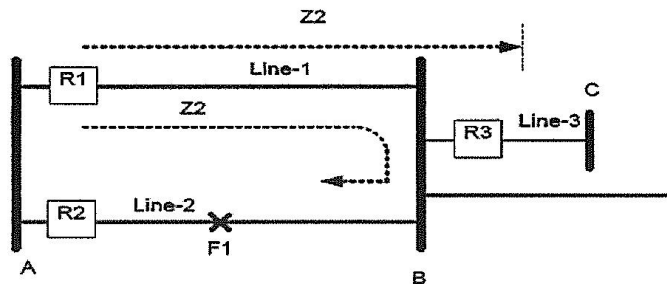


Fig.3a

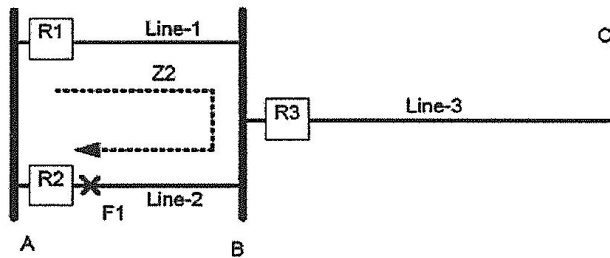


Fig.3b


3 2

(20 Marks)

a) *Put True or False:*

- Speed of protection so important (*Discuss* your answer).[5]
- A distance relay is said to over-reach when the apparent impedance presented to it is less than the impedance to the fault.[3]

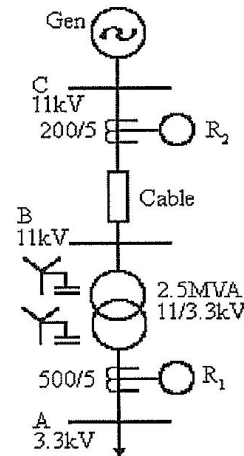b) Consider the feeder shown in Fig. 4 with earth fault relays R1 and R2. Relay R1 is used for providing protection against earth fault at the secondary side of 2.5 MVA, 11/3.3 kV transformer, whereas, relay R2 has to provide protection at bus B. A 200:5 CT is connected to inverse over-current relay R2 and 500:5 CT ratio is connected to R1.



- **Compute** the setting of standard inverse unit at relay R1. Assume that maximum system unbalance is 20% and SLG fault current at bus A is 480 A and at bus B it is 650A? [6]
- **Compute** the time required by relay R2 to clear SLG fault at bus B? [6]
 - Use coordination time margin of 0.3sec.

Fig.4

Question (4):

(20 Marks)

a) *Define*: Fuse coordination, Characteristic quantities and Energizing quantities. [9]

b) For the system shown in Fig. 5. **Design** the three zone step for the distance relay R_b . **Given** From short-circuit study that $I_2/I_1 = 0.5$. [11]

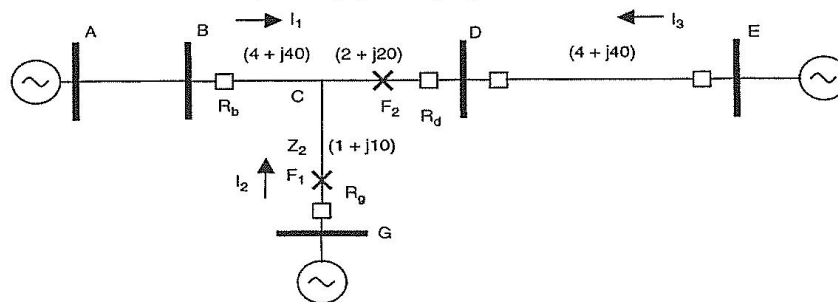


Fig.5

Question (5):

(15 Marks)

- a) *What* are bouholz relay and the significance of it in to the transformer? [9]
- b) *When* voltage increases then current also increases then *what* is the need of over voltage relay and over current relay? *Can* we measure over voltage and over current by measuring current only? [6]

With my best wishes
Dr.Eman Saad