Kafrelsheikh University Faculty of Engineering

Department: Electrical Engineering Year: 4th Power Systems & Machines

Subject: Electric Power systems analysis II



Final Exam- January 2016 Time allowed: 3 hours

(30 marks)

Full Marks: 100 Pages: Two pages Date: 16/01/2016

Attempt to solve the following problems

a) What are the meant by:

Power system instability, swing equation, equal area criteria, security levels, power system basic requriments and blackouts.

b) In the system shown in Figure 1, a three phase static capacitor of 0.05 per unit, at a base MVA equals 100, is connected through a switch S. <u>Negeclt</u> the effects of static load.

<u>Calculate</u> the steady state limit, with suitable techically and economical comments for two positions for the capacitor placment which are at the mid point of the upper line only and at the motor bus.

- 1) If the switch is open.
- 2) When the switch is closed.
- 3) If the primiary voltages of the motor transformers equal 1.3 p.u.
- 4) If the static capacitor is replaced by an inductor with the same reactance.
- 5) If the capacitor is inserted inseies with the generator.
- 6) If a three phase fault occurred at point F when case 2 is considered.

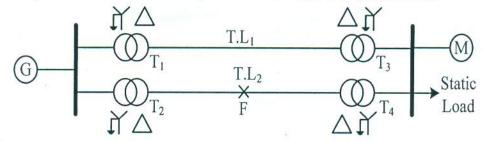


Figure (1)

Generator	15MVA, 11 kV, x ₁ =0.14 p.u., x ₂ =0.15 p.u., x ₀ =0.04, x _n =0.1 p.u.
Motor	15 MVA, 11 kV, x ₁ =0.18, x ₂ =0.20 p.u. x ₆ =0.1 p.u., x _n =0.2 p.u.
T_1, T_2	5 MVA, 11/66 kV, x=0.12 p.u.
T3, T4	5 MVA, 66/11 kV, x=0.12 p.u.
T.L ₁ , T.L ₂	5 MVA, x ₁ =x ₂ =0.2 p.u., x ₆ =0.6 p.u.

2

(20 marks)

- a) <u>Discuss</u> the recent trends that used to enhance steady state and transient stability.
- b) Consider a three phase symmetrical fault at point F, <u>deduce</u> the formula critical clearing angle in terms of the stability limits for pre-during and post fault.
- c) <u>Obtain</u> the critical clearing angle for the system shown in Figure 1 for a three phase fault at the point F. The generator is delivering 1.25 per unit power under pre-fault condition.

or stable		
or stable		
ter certain		
ole voltage		
generator		
ossible to		
4.		
on.		
equivalent		
nce of 1.1		
age of the		
erator emf		
5 marks)		
78		
tor.		
al annual		
1.5 % as		
insurance. <u>Determine</u> a suitable two parts tariff if the losses in the transmission and		
sume that		
nual load		

Best wishes Dr. Ragab A. El Sehiemy Dr. Eman Saad