





Q3:

(25 Mark)

(a) Explain the four quadrant operation of dc chopper drive; support your answer with needed wave forms?

(b) A dc chopper controls the speed of a dc series motor. The armature resistance,  $R_a = 0.04 \Omega$ , field circuit resistance,  $R_f = 0.06 \Omega$ , and back emf constant,  $k_v = 35$  mV/rad/s. The dc input voltage of the chopper,  $V_s = 600$  V. If it is required to maintain a constant developed torque of  $T_d = 547$  N.m, plot the duty cycle,  $k$ , of the chopper against the motor speed.

Q4:

(20 Mark)

(a) Explain the voltage, current and frequency control method of induction motor.

(b) A three phase 35 hp, 4-pole, 50 Hz, 1450 rpm, Y-connected induction motor has the following parameters:  $R_s = 0.2 \Omega$ ,  $R_r = 0.22 \Omega$ ,  $X_s = 1.2 \Omega$ ,  $X_r = 1.8 \Omega$ , and  $X_m = 13 \Omega$ . The motor is controlled by current source inverter and  $I_i = 47$  A. if the frequency is 38 Hz and  $T_d = 140$  N.m. determine: (i)  $s_{mT}$ , (ii)  $T_m$ , (iii)  $\omega$ , (iv)  $V_a$ , (v)  $s$ , (vi)  $pf$ .

*With my best wishes*

*Dr. Eng./ Mohamed I. Abd EL Wanis*