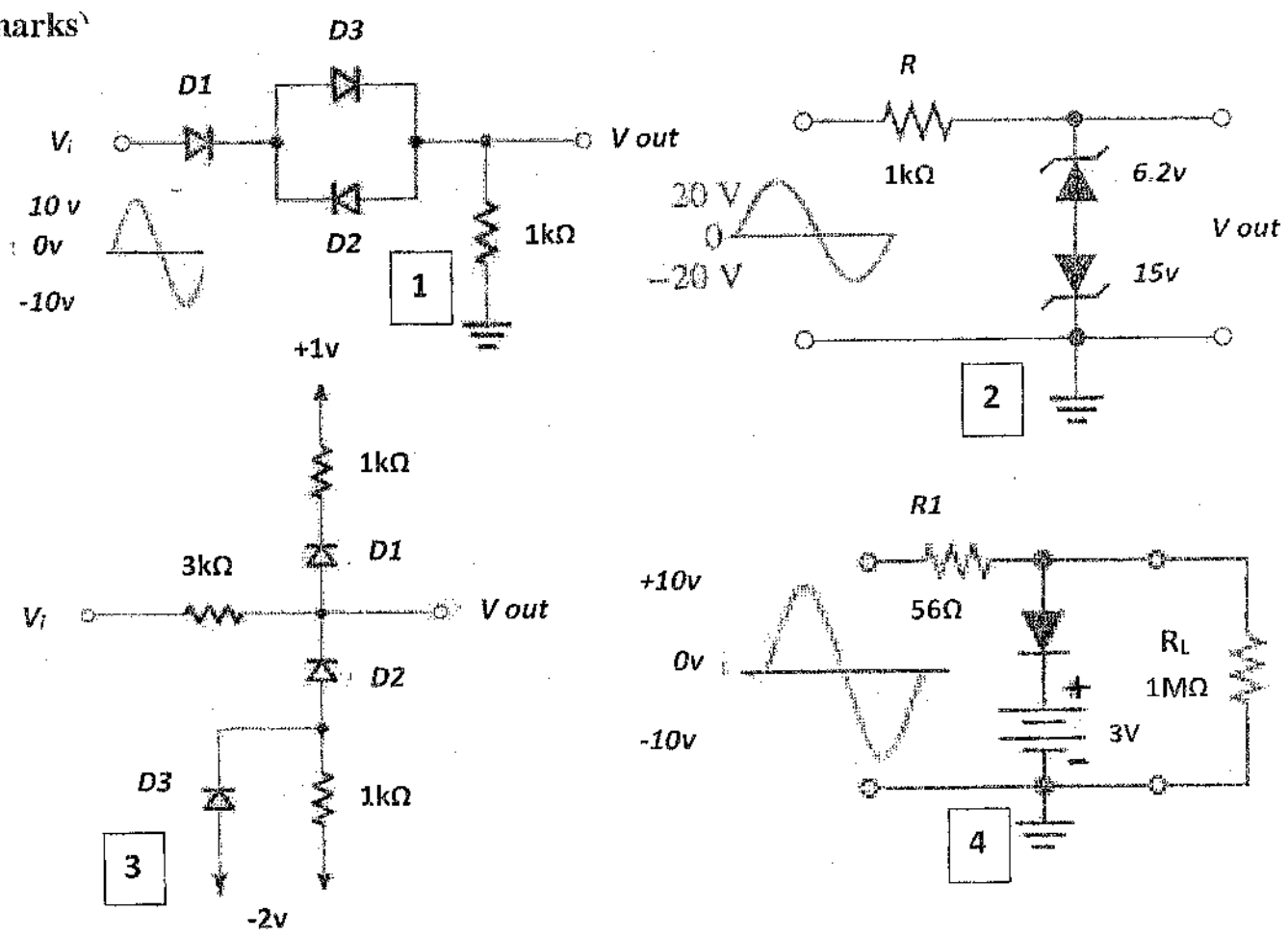




This exam measures ILOs no: a3, a4, a5,a8 ,a14, b6,c7

**[1] Question One: (24 Mark)**

- A) Derive an expression for AC- Resistance. (4 marks).
- B) sketch diagram of dc power supply, then answer the following questions: (8 marks).  
 - Defines the function of each component within the diagram.  
 - Sketch the input and output of each component.  
 - Explain the full wave rectification by using high PIV diodes, what PIV rating is required for the diodes and the ripple factor for the filtered output.
- C) Determine  $v_{RL}$  (RL voltage) for each network of shown below for the same input shown. (12 marks)




**[2] Question Two: (21 Mark)**

A) To obtain the hole drift current one and half of the electron drift current, how should the carrier densities to obtain?  $\mu_n=1350 \text{ cm}^2/\text{v}\cdot\text{sec}$ ,  $\mu_p=480 \text{ cm}^2/\text{v}\cdot\text{sec}$  (7 marks).

B) For the following figure answer the following: (6 marks)

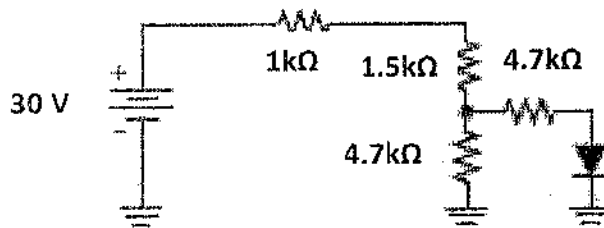1. Whether the silicon diode is forward-biased or reverse-biased.
2. The voltage across the diode in Figures, assuming the practical model.
3. The voltage across the diode in Figures, using the complete diode model with  $r_d = 10 \Omega$  and  $r_R = 100 \text{ M}\Omega$ .



B) Sketch the reverse biased pn junction, the calculate the junction capacitance of a pn junction consider a silicon pn junction at  $t=300^{\circ}\text{k}$ . With doping concentration of  $N_d=10^{16} \text{ cm}^{-3}$  and  $N_a =10^{15} \text{ cm}^{-3}$ , assume that  $n_i=1.5 \times 10^{10} \text{ cm}^{-3}$  and let  $C_{j0}=0.5 \text{ Pf}$  and  $V_R=5 \text{ v}$ . (8 marks)

=====



This exam measures ILOs no: a2, a3, a6, a8, a14, b3, c4

Answer all the following questions

- 1-) For Fig. (1), find the current  $I_2$  and the voltage  $V_{ab}$ . [ 8 Marks]
- 2-) For Fig. (2), find the current through  $R_1$  by using superposition theorem. [ 15 Marks]
- 3-) For Fig. (3), find the current through each element by using the supermesh analysis approach. [ 11 Marks]
- 4-) For Fig. (4), determine the nodal voltages by using the supernode approach. [ 11 Marks]

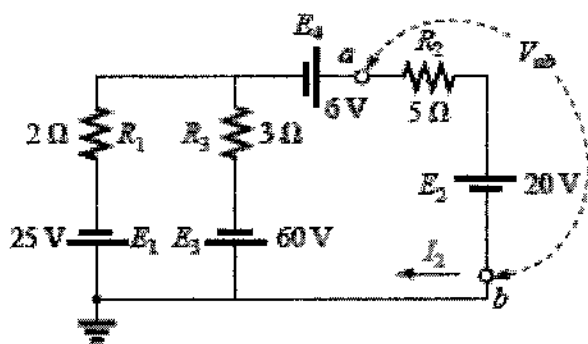


Fig. (1)

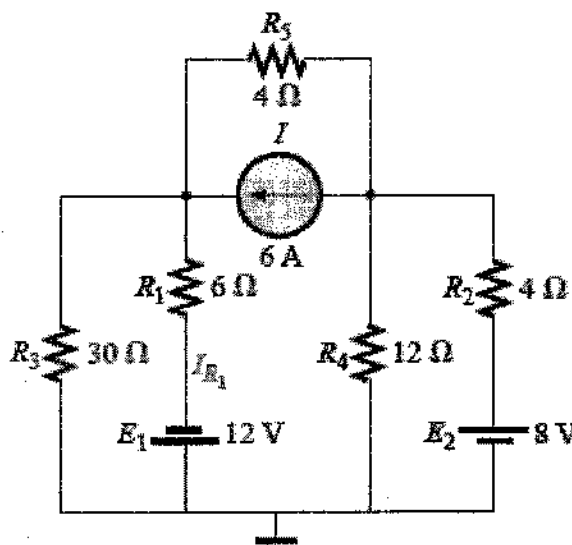


Fig. (2)

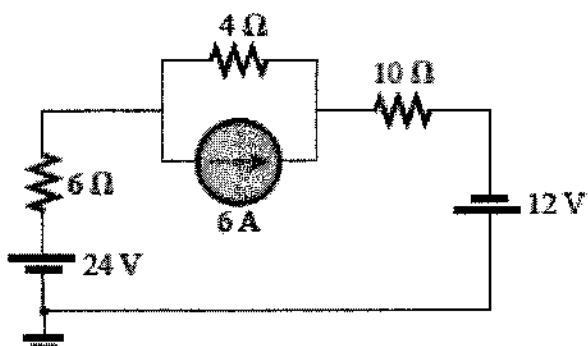


Fig. (3)

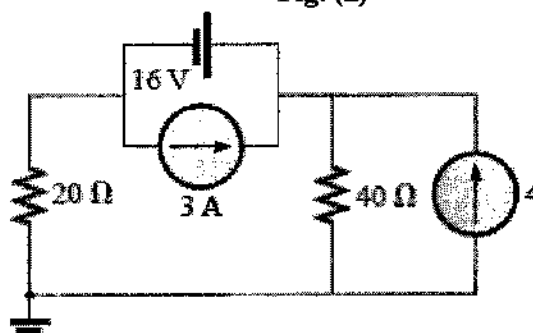


Fig. (4)

With my best wishes  
 Dr. Sherif Emam