


| | | |
|--|--|--|
| Ministry of Higher Education and Scientific Research Faculty of Engineering Kafrelsheikh University |  كلية الهندسة | وزارة التعليم العالي والبحث العلمي كلية الهندسة جامعة كفر الشيخ |
| First-term Examination of Academic Year 2019/2020 | | |
| Department: Electrical Engineering | Year: Third year | Total Marks: 85 |
| Course Title: Electronic Measurements and Testing (1) | Course Code: ECE 3006 | Term: First Term |
| Date: Jan. 15 - 2020 | Number of questions: 4 | Allowed Time: 180 Minutes |

Answer the following questions

Illustrate your answers with sketches when necessary

Question 1

(20 Marks)

- I. Given figure 1, derive and sketch the voltage transfer function of that passive RC filter. (7 Marks)
- II. Given figure 1, design that filter with cut-off frequencies of 160 Hz and 8 kHz. The load for this circuit is 1 MΩ. For good design purpose, filter output resistor should be one tenth of load resistor and its input resistor should be one tenth of its output resistor. (6 Marks)
- III. We have an amplifier that amplifies a 1 kHz signal from a detector. The load for this amplifier can be modeled as a 50 kΩ resistor. The amplifier output has a large amount of 60 Hz noise. We need to reduce the amplitude of noise by a factor of 10. Design a first-order passive filter which can be placed between the amplifier and the load and does the job. (7 Marks)

Question 2

(25 Marks)

- I. Derive an expression for the output voltage difference v_{D2D1} , Fig.2, as a function of the input voltage difference v_{G2G1} . (5 Marks)
- II. Modify the MOS differential-pair configuration and prove that it can be used as analog multiplier with temperature dependent term. (10 Marks)
- III. Explain and prove how you can eliminate the temperature dependent term. (10 Marks)

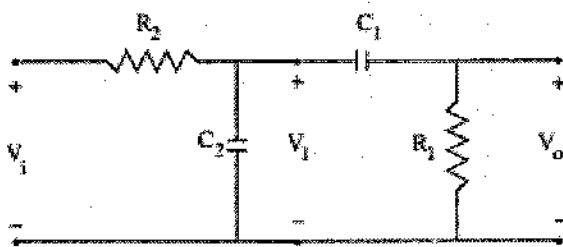


Figure 1

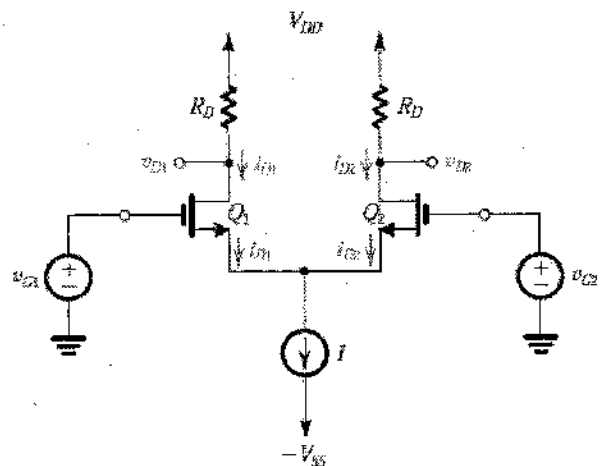


Figure 2

Question 3

(20 Marks)

Suppose that the modulating signal $m(t)$ is a sinusoid of the form $m(t) = a \cos \omega_m t$ with the carrier signal $c(t) = A \cos (\omega_c t + \phi_c)$ $\omega_m \ll \omega_c$

- I. Determine and sketch the DSB-SC AM signal and its upper and lower sidebands in both time and frequency domain. (5 Marks)
- II. determine the power-spectral density of the modulated signal, the power in the modulated signal, and the power in each of the sidebands. (5 Marks)
- III. Given Figure 3 and same modulating signal, Drive an expression of output signal in time and frequency domain (5 Marks)
- IV. State the advantages and disadvantages of figure 3 scheme as compared to DSB-SC AM scheme (5 Marks)

Question 4

(20 Marks)

- I. Given figure 4, drive the transfer function of the feedback network, closed loop gain of the opamp, and oscillation frequency. (10 Marks)
- II. Given Figure 4, design the circuit to generate 1 KHz. Assume any necessary resistors values. (10 Marks)

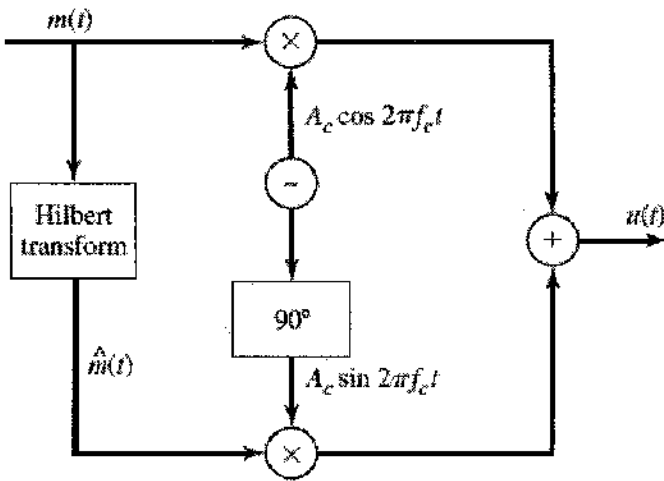


Figure 3

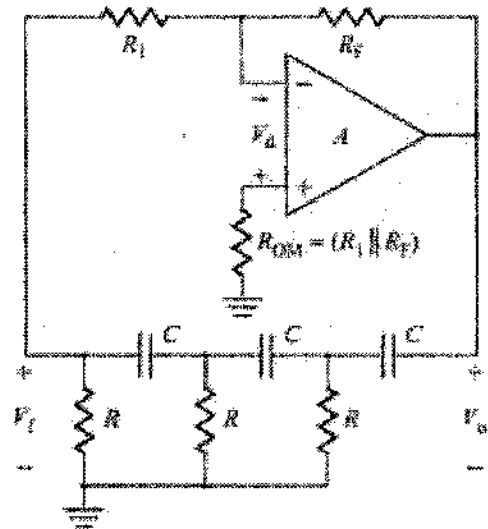


Figure 4