Kafrelsheikh University Faculty of Engineering Department of electrical eng.

Subject: Tests and electronic Measurements(1)

Examiners: Dr. Bedir B. Yousif Dr. Shamya Ghamry



Date: 9/1/2019

Time allowed: 3 Hours Full mark: 85 Mark Final term: Two pages, Academic code: ECE3006

3rd year, communications

Course ILOs

Field	National Academic Reference Standards (NARS)			
	Knowledge & Understanding	Intellectual Skills	Professional Skills	General Skills
academic standards that the course contribute in achieving it	a.4, a. 5. , a.6 , a.8 ,a.12 , a.13 a.14 , a.17, a.23 and a.26	b.2, b.3, b.4, b.5, b.6, b.8, b.9, b.11, b.12, b14, and b.16	c1 , c.3 ,c.4,c.5, c.6, c.15, c.16, c.17 and c.18	d.1, d.3, and d.6,


Solve the following questions:-**Ouestion One:- (42 Mark)**

1. Design a third order unity gain butterworth low pass filter with the corner frequency of 50 KHz. The coefficients of butterworth design are given as $a_1=1$, $b_1=0$, $a_2=1.618$, $b_2=1$, $a_3=0.618$, $b_3=1$. (8 M)

2. State the experimental steps that are followed to draw the frequency response of a certain filter.

3. Write down a general form of low pass filter transfer function and indicate the meaning of each term. (8 M)

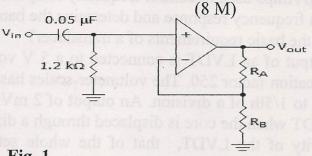4. Analyze the circuit in Fig. 1 to decide the type of the filter and its cut off frequency.




	rig. 1	
Choose the correct answer	e is son to at 50°C and 4 kC	(10 M)
A filter i	rejects all frequencies within	a specified band and passes all
those outside this ba	and.	are 3001 has 3001 assumed
a. Low pass	b. high pass c. band pass	d. band stop
'he bandwidth in a _	filter equals the cut of	off frequency.
a. Low pass	b. high pass c. band pass	d. band stop
ilters with the	characteristic are useful	when a rapid roll-off is required
a. Butterworth	b. Chebyshev	c. Bessel
		Page 1/2

5/1/201

4. Which filter exhibits a linear phase characteristic? a. Butterworth b. Chebyshev c. Bessel d. all of them 5. Filters with the characteristic provide a very flat amplitude in the passband a. Butterworth b. Chebyshev c. Bessel

Question Two:- (43 Mark)

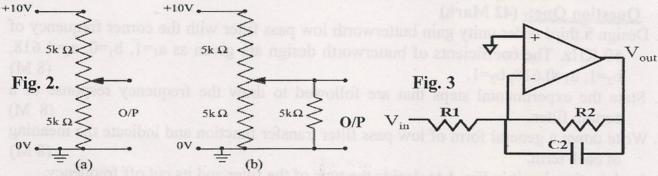- 1. State the main differences between (6 M)a- Graded index and step index fiber. b-Second and third windows in optical fiber communications.
- 2. Why optical fibers communication has greater transmission bandwidth than the conventional communication systems? (6 M)
- 3. What are the main differences between transducers and sensors? (6 M)
- 4. For potential resistance transducer in Fig. 2. Calculate the output voltage in each case in Fig. 2(a,b). and what the effect of load resistance? (6 M)



- 5. Ideal Op Amps used to control frequency Response for the circuit in Fig. 3, plot the gain frequency response and determine the bandwidth. (6 M)
- 6. Expain the basic requirements of a transducer? (4 M)
- 7. The output of an LVDT is connected to a 5 V voltmeter through an amplifier of amplification factor 250. The voltmeter scales has 100 divisions and the scale can be read to 1/5th of a division. An output of 2 mV appears across the terminals of the LVDT when the core is displaced through a distance of 0.5 mm. Calculate :the sensitivity of the LVDT, that of the whole set up, and the resolution of the instrument in mm.
- 8. The resistance of a thermistor is 800 Ω at 50°C and 4 k Ω at the ice-point. The characteristic constants (A, B) for the thermistor and the variations in resistance between 30°C and 100°C are
- 9- Drive an expression for Poisson's ratio and gauge factor in strain gauges sensors

Best wishes of success Dr. Bedir yousif

Page 2/2