

- C- State and explain an experimental tool that can be used to detect and specify the errors in the received signals in case of M-ary PSK and M levels QAM. (3-marks)
- B- An input data stream "0110010110011" is passed through a line encoder circuit, the oscilloscope is used to see the output stream, draw the signal that will be seen in case of . (3-marks)
- A- Identify the desired properties of line codes (4-marks)
- i- BRZ    ii- Manchester    iii- Differential encoders
- Draw the circuit diagram of one of these encoders
- C- Draw the circuit diagram of one of the encoders

**12) Question Two: (10 Mark) [measures ILos of a15 and b15]**

- B- Write down the general equation for PAM spectrum specifying each term. (2-marks)
- A- i- Explain, with the aid of sketches and diagrams the operation of delta modulation system. (5-marks)
- ii- Consider a delta system designed to accommodate analog signals limited to bandwidth of 5KHz. A sinusoidal test signal of amplitude of 1V and frequency of 1KHz is applied to the system. The sampling rate of the system is 50 KHz. Calculate the step size to minimize the slop over load and then determine the signal to quantization noise ratio for this test. (3-marks)
- C- Draw the circuit diagram for non-coherent FSK demodulator and specify the output of each stage

**11) Question One: (10 Mark) [measures ILos of a15, b15, b16 and c18]**

Answer the following questions:

**This Exam measures the ILos /a8, a15, b15, b16 and c18/**

**[3] Question three: (10 Mark)** [measures ILOs of a8 and b16]

A- Explain the Cathode Ray Tube and then explain J.J. Thomson Cathode Ray tube Experiment. (4-marks)

B- How can be Build a Current Mirror Circuit with illustration the importance of caveat for current mirror circuit? (Sketch the circuit diagram). (4-marks)

C- Define the power electronic devices, then compare between the small signal diode and shottcky diode. ( 2-marks)

**[4] Question four: (10 Mark)** [measures ILOs of a8 and b16]

A- Sketch the circuit diagram of Vacuum Tube Audio Amplifier and explain the following ( 5-marks)

- One of the problems with building vacuum tube circuits.
- Why using two coupling capacitors instead of just one adds?
- Electronic tubes devices used sockets, why?

B- Design high voltage plate dc power supply at 170 volts. What the bad aspect of using an ignition coil. ( 3-marks)

C- Compare between the traditional tube and microwave tubes? ( 2-marks)

Best Wishes

Committee of Correctors and Testers

Dr. Noha El-shalaby

Dr. Shamia Ghamry

page(2/2)