

2018/5/27




Kafrelsheikh University  
Faculty of Engineering  
Department of Electrical Engineering  
Year: 3<sup>rd</sup> comm. Academic Number:  
Name: ECE 3209

Date: 27/5/2018  
Time allowed: 3h  
Full Mark: 100 degree  
Final Exam: 2 page  
Subject: Electronic circuits 2

This exam measures ILOs no: a.4, a.8, a.13, a.14, a.15, b.2, b.5, b.16, c.13, c.17, d7

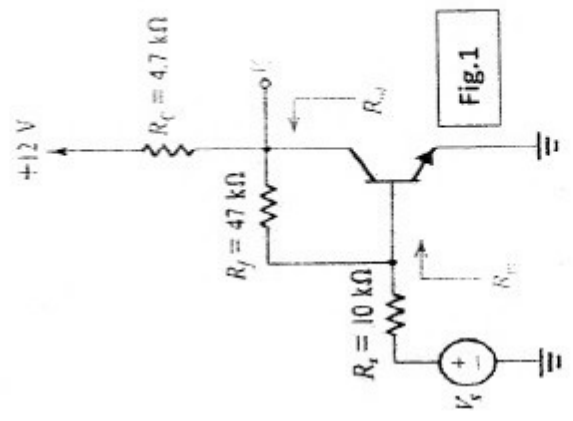**[1] Question One [22 degrees]:**

- 1- Explain the power Amplifiers classes, power efficiency and then explains the power considerations of series fed class A amplifier. [10 degrees]
- 2- Determine the equivalent circuit, small-signal voltage gain  $V_o / V_s$ , the input resistance  $R_{in}$ , and the output resistance  $R_{out} = R_{of}$ . The transistor has  $\beta = 100$ , for the fig.1. [12 degrees]




**[2] Question Two [22 degrees]:**

- 1. Find the equivalent circuit for the following:
  - a. Voltage series F.B. connection. [6 degrees]
  - b. Voltage shunt F.B. connection using FET. [6 degrees]
- 2. Analysis the RC phase shift oscillator, to get an expression of its resonance frequency when  $1 - R \neq R_L$ . 2-  $R = R_L$ . [10 degrees]

**[3] Question Three [20 degrees]:**

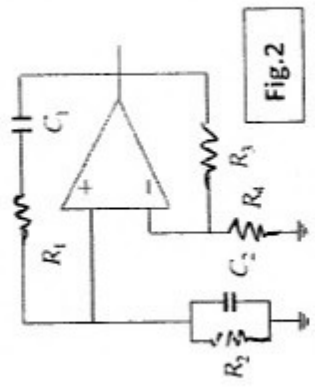- 1. Analysis the crystal oscillator, to get an expression of its resonance frequency, then explains the characteristics of the quartz crystal [8 degrees].
- 2. Design an oscillator circuit using a crystal oscillator with an operation amplifier, and then define this type of oscillator. [6 degrees].
- 3. Determine the value of capacitance  $C_1$  and  $R_1$  if  $R_2 = 10k\Omega$ ,  $C_2 = 0.1mF$ ,  $R_3 = 10k\Omega$ ,  $R_4 = 1k\Omega$  in the Wien bridge oscillator shown has an output frequency of 1kHz as shown in Fig.2. [6 degrees]




**[4] Question Four [20 degrees]:**

1. Drive an expression of the ripple factor of capacitor filter [7 degrees].

2. Design and explain a Op-Amp series regulator. [6 degrees].

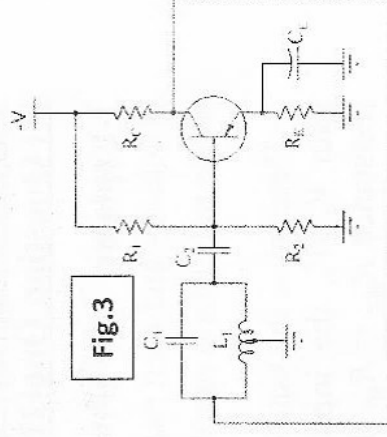
3. Calculate the operating frequency of the following oscillator circuit, if  $C_1 = 0.033 \mu\text{F}$  and  $L_1 = 175 \text{ mH}$ , then Calculate the operating frequency of the following oscillator circuit, if  $C_1 = 0.047 \mu\text{F}$  and  $L_1 = 150 \text{ mH}$ . . as shown in Fig.3 [7 degrees].



**[5] Question Five [16 degrees]:**

1. Define the Multivibrator and its type, Sketch the block diagram of transistor Bistable Multivibrator and explain its operation. . [10 degrees].

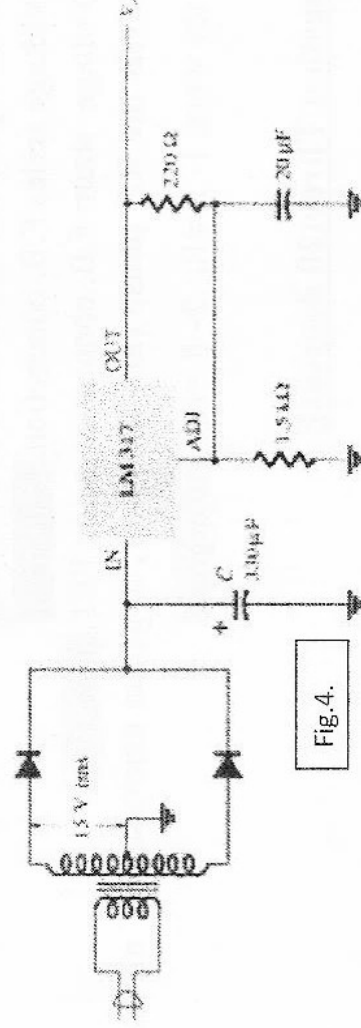2. Determine the regulated output voltage from the circuit of Fig.4. [6 degrees].



**[\*] Question [5 degrees]:**

Write about one of the following:

1. Super capacitor.
2. Nano technology.
3. Electronic papers.
4. Opt coupler and opt isolator.