



Kafrelsheikh University
Faculty of Engineering
Department of Electrical Engineering
Year: 3rd communication

Date: 23/ 5 /2018
Time allowed: 3h
Full Mark: 85 degree
Final Exam: 2 page

Subject: Electronic Measurements & Testing(1), ECE3006

Academic Number:

Name:

This exam measures ILOs no a.4, a. 5, a.6, a.8, a.12, a.13 a.14, a.17, a.23 and a.26 b.2, b.3, b.4, b.5, b.6, b.8, b.9, b.11, b.12, b.14, and b.16 c1, c.3, c.4, c.5, c.6, c.15, c.16, c.17 and c.18 d.1, d.3, d.6.

Question 1 (25) Degrees

- Design** a notch filter at $f_c=100$ Hz, and $k_{PB}=1$. (9 degrees)
- Sketch Nyquist** criterion to determine the stability of the open loop gain. $A\beta(S)=2/S(S+1)(2S+1)$ by gain margin. Then estimate the range of stability with unity feedback by Routh. (9 degrees)
- Sketch a block** diagram for a practical phase shift oscillator for amplifier stabilization at 6.5GHz, Explain the function of each component. (7 degrees)

Question 2 (17) Degrees

- Sketch a block** diagram for a practical implementation of the active filter tuned oscillator. **Explain** the function of each component. (9 degrees)
- Sketch a block** diagram of pierce oscillator, **explain** the principle operation of it briefly. (8 degrees)

Question 3 [measures ILOs of a4, a8, a14, b4 and b5]

- Explain with aid of sketches, the demodulation of AM using rectifier detector.
- Sketch the modulator and demodulator block diagrams of the single side band amplitude modulation
- The AM signal : $s(t) = A_c [1 + k_a m(t)] \cos(2\pi f_c t)$ is applied to the system in figure 1. Assuming that the message signal is limited to the interval $-W \leq f \leq W$ and the carrier frequency $f_c > 2W$ show that $m(t)$ can be obtained from the square rooter



Fig.1

- d- A DSB-SC AM signal is modulated by the signal : $m(t)=2 \cos 2000\pi t$. The carrier signal is $c(t)=100 \cos 2\pi \times 10^6 t$
- Sketch the modulated signal in time domain.
 - Determine and sketch the spectrum of the AM signal.
 - Calculate the average power of the AM signal.

Question 2/measures ILOs of a14, b4, b5,b8, b12,c1 and c5]

- Explain, with aid of diagram, the demodulation of WBFM using phase locked loop (PLL).
- The carrier $c(t)=A \cos 2\pi 10^6 t$ is angle modulated (PM or FM) by the sinusoid signal $m(t)=2 \cos 2000\pi t$. The deviation constants are $k_p=1.5$ rad/V and $k_f=3000$ Hz/V.
 - Write general form equation in each case.
 - Determine the bandwidth in each case
- A signal $m(t)$ band limited to 5 kHz is sampled at a rate 30% higher than the Nyquist rate. The maximum acceptable error in the sample amplitude is 0.5% of the peak amplitude. The quantized samples are binary coded. Find the minimum band width of the channel required to transmit the encoded binary signal.