

- Books & notes are not allowed. * Any missing data could be reasonably assumed.
- Course ILOS (مخرجات التعلم المستهدفة من مقرر الهندسة الالكترونية)

Field	National Academic Reference Standards (NARS)			
	Knowledge & Understanding	Intellectual Skills	Professional Skills	General Skills
Academic standards that the course contribute in achieving it	a3, a4,a5,a8 ,a14	b2, b6, b8, b16	c2,c3	d1,d7

Solve all the following questions:-

Question One: (30 Mark) (a3,a4,b2,c2,d1)

a- Calculate V_o in the circuit of Fig. 1.

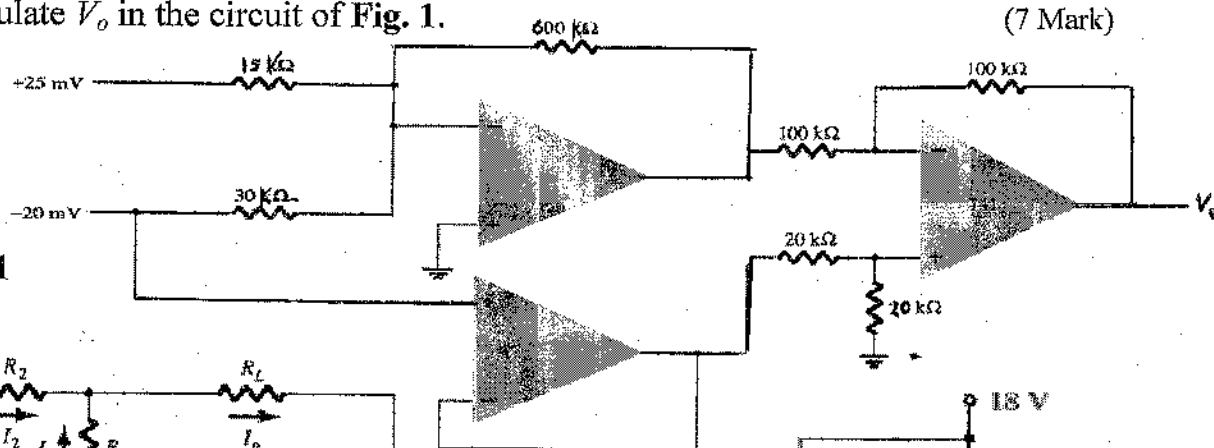


Fig. 1

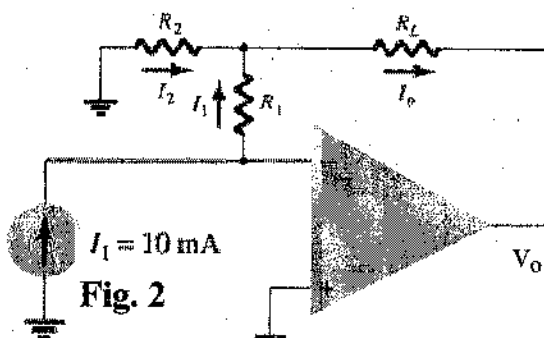


Fig. 2

b- Find V_o and I_o in the circuit of Fig. 2.

If $R_1 = 20 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$ and $R_L = 4 \text{ k}\Omega$ (7 Marks)

c. For the network of Fig. 3: Evaluate Z_i , Z_o , A_v and A_i . (8 marks)

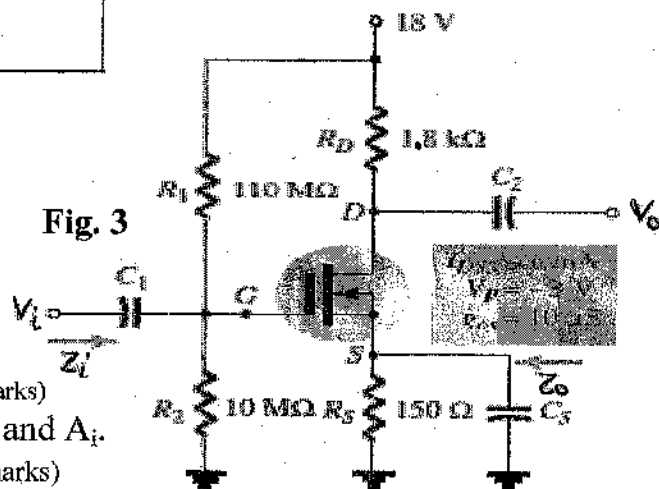


Fig. 3

d. For the voltage-divider bias configuration

of Fig. 4, if $V_D = 12 \text{ V}$, $V_{GS\text{off}} = -3.78 \text{ V}$ and $I_{DSS} = 10 \text{ mA}$, calculate the value of R_S . (8 marks)

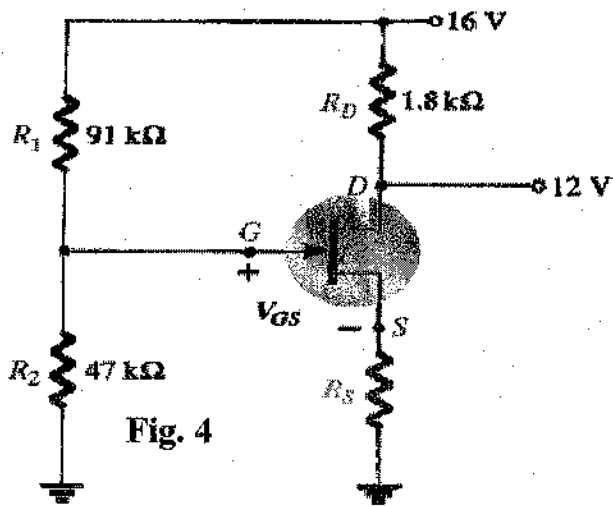


Fig. 4

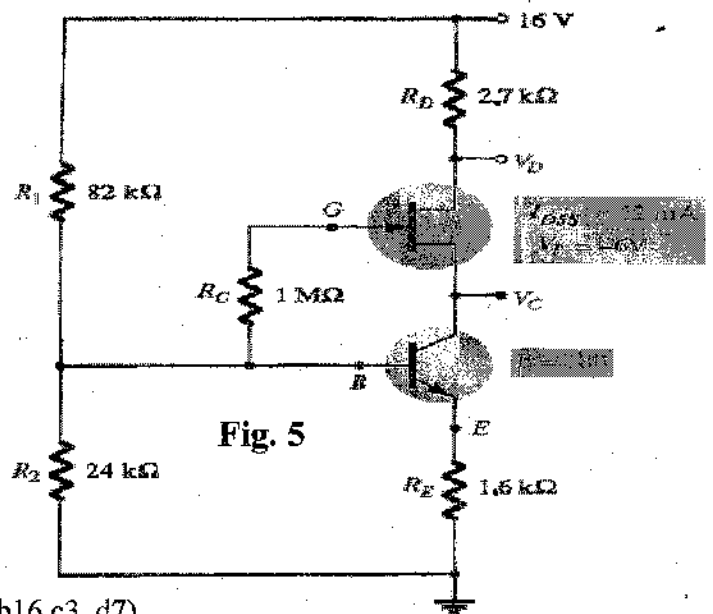


Fig. 5

Question Two: (40 Mark) (a5,a8,a14,b6,b8,b16,c3, d7)

- a- Determine the levels of V_D and V_C for the network of Fig. 5 . (10 marks)
- b- Choose the values of R_D and R_S for the network of Fig. 6 that will result in a gain of 8 using a relatively high level of g_m for this device defined at $V_{GSQ} = \frac{1}{4}V_P$. (10 marks)

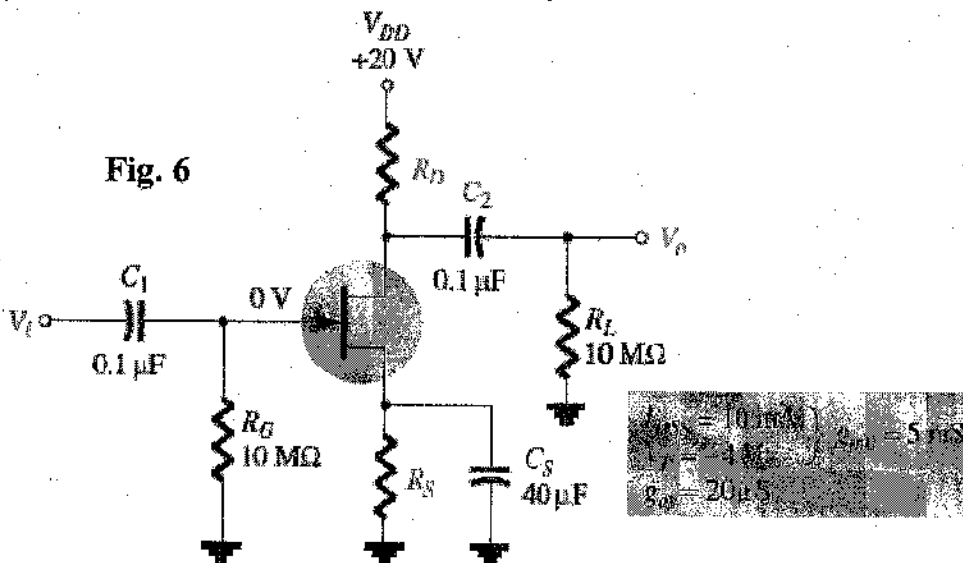


Fig. 6

- c- Implement a boolean logic function $Y = \overline{AB} + C$ using CMOS transistors? (7 marks)
- e- An analog switch is used to sample a signal $x(t) = 10 + 5\cos 2000t + 8\cos 8000t$. Determine the minimum frequency of the pulses applied to the MOSFET gate. (5 marks)
- f. Design an analog time division multiplexer for a four input sinusoidal signals with frequencies of $f_1 = 5$ kHz, $f_2 = 10$ kHz, $f_3 = 15$ kHz and $f_4 = 20$ kHz, and peak amplitude 3 V to be transmitted on the line? Furthermore draw the input output waveforms and gating rectangular signal of 40KHz? Hint: MOSFET device has $V_{GS(th)} = 2$ V and lossless (8 marks)

Best wishes of success
Dr. Bedir yousif