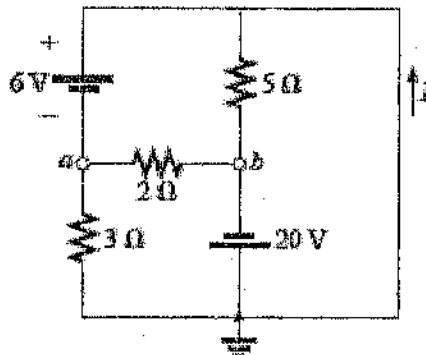





Based on ECE1001 course specification ILOS

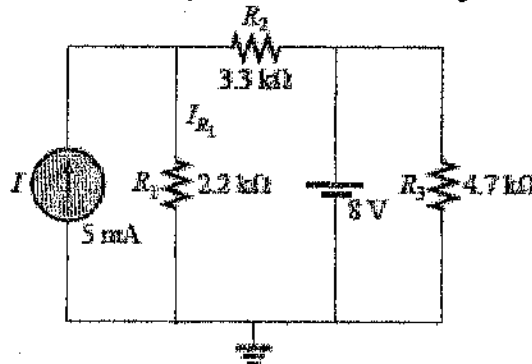Question No. 1 [15 Marks]

- A-) By using Kirchhoff's voltage law, determine the voltage V_{ab} . [4 Marks]
 B-) Calculate the current I . [4 Marks]




- C-) Using superposition, find the current through R_1 for the following network. [7 Marks]



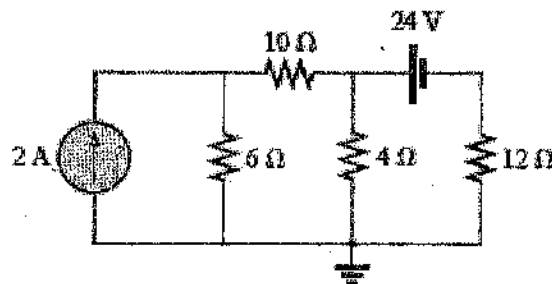Question No. 2 [20 Marks]

- A-) Using Nodal analysis method, determine the current through 12Ω resistor of the following network. [8 Marks]




Dr. Sherif
Dr. Noh




Based on ECE1001 course specification ILOS

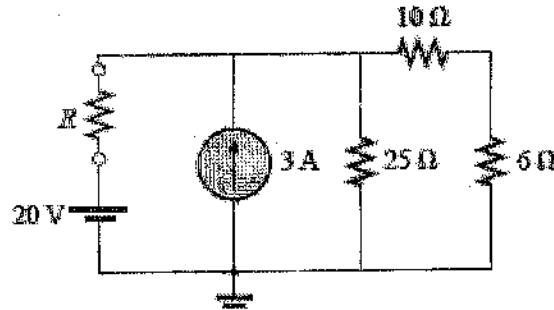B-) Find the Thévenin equivalent circuit for the network external to the resistor R in the following Circuit: [8 Marks]




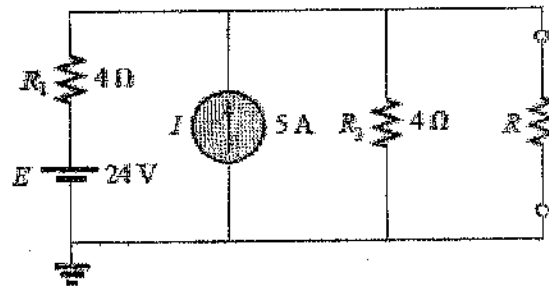C-) For the following network, determine the value of R for maximum power to R , and determine the maximum power to R [4 Marks]



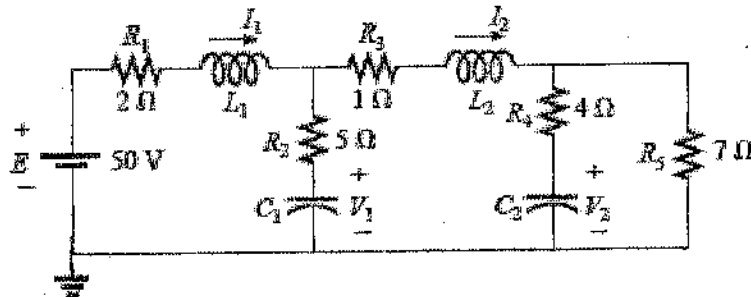Question No. 3 [10 Marks]

A-) Find the currents I_1 and I_2 and the voltages V_1 and V_2 for the network of the following Fig.: [10 Marks]



With my best wishes

Dr. Sherif Imam