

اداء كويس

٥٦


Kaferelsheikh University  
Faculty of Engineering  
Electrical Engineering Dept.  
Final Exam, 2016-2017  
Date: 2/1/2017



Subject: Electronic  
Time : 90 minuets  
Full Mark: 45 degree  
Year: First  
Exam in 2page

**[1] Question One: (25 Mark)**

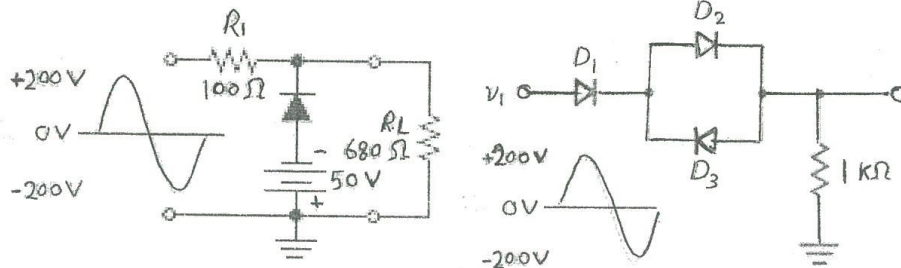- A) Distinguish between majority and minority carriers in a semiconductor. Define mobility of charge carriers.
- B) Discuss how a depletion layer is formed in a P-N diode and how does it vary with biasing? Draw V-I characteristics of P-N junction diode.
- C) Derive an expression for the conductivity of a semiconductor.
- D) Determine  $v_o$  ( $R_L$  voltage) for each network of shown below for the input shown.



- E) source injects charge carriers into semiconductor bar. explain how current flow, what is this current?

**[2] Question Two: (10 Mark)**

- A) sketch diagram of dc power supply (with reference to the function of each component within the diagram).
- B) explain, full wave rectification using two diode? what is the difference between this method and using bridge?
- C) compare between dynamic resistance and static resistance.

تابع باقى الاسئله فى خلف الورقه

with best wishes

Dr. noha abd al salam

G

D) Find the resistivity of (a) intrinsic silicon and (b) n type silicon with  $N_A = 10^{16}/\text{cm}^3$ . Use  $n_i = 1.5 \times 10^{10}/\text{cm}^3$ , and assume that for intrinsic silicon  $\mu_n = 1350 \text{ cm}^2/\text{V-s}$  and for,  $\mu_p = 480 \text{ cm}^2/\text{V-s}$  and for the doped silicon,  $\mu_n = 1110 \text{ cm}^2/\text{V-s}$  and,  $\mu_p = 400 \text{ cm}^2/\text{V-s}$ .

E) Determine the peak output voltage, what PIV rating is required for the diodes and the ripple factor for the filtered bridge rectifier with a load as indicated in Figure

