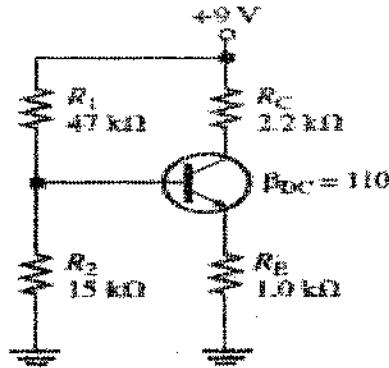


Question (1):


(40 marks)

Put (✓) or (✗) and explain the reason for both cases then correct the false one:

- 1- For the voltage divider biasing circuit shown, the value of the base voltage with respect to ground equal 2.04 V.




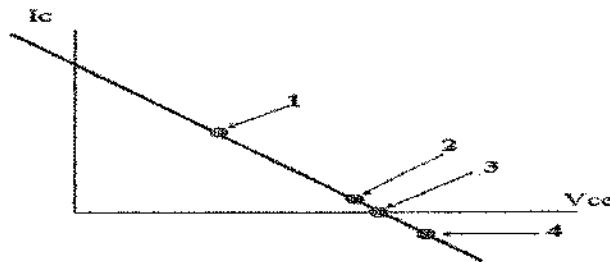- 2- The load line shown below explains many points of amplifier's operation, the type of power amplifier in point (4) is Class A.




- 3- The voltage follower is a special case of a noninverting amplifier configuration as it has the same impedance formula but with $B=1$.

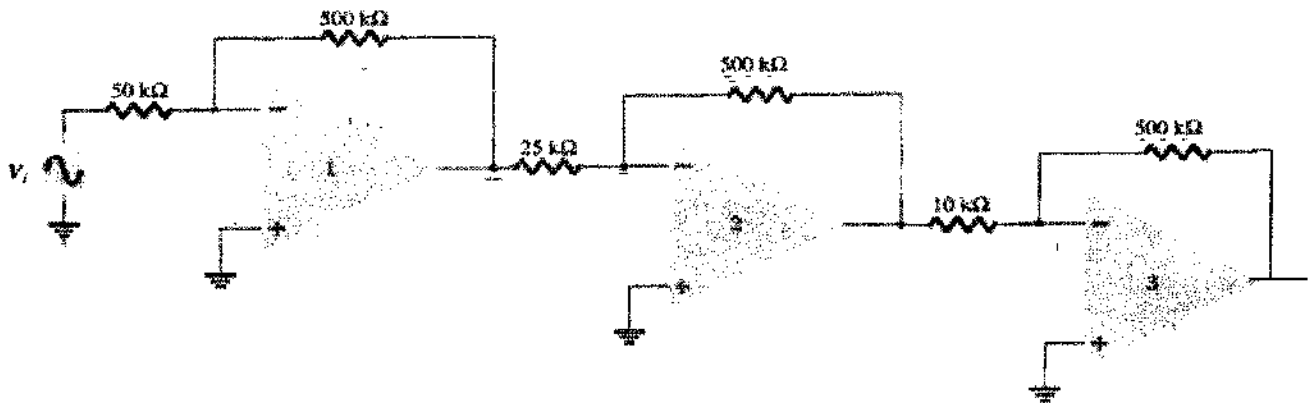- 4- The connection of three op-amp stages shown below used to provide outputs that are 10, 20, and 50 times larger than the input, as a feedback resistor $R_f = 500 \text{ k}\Omega$.




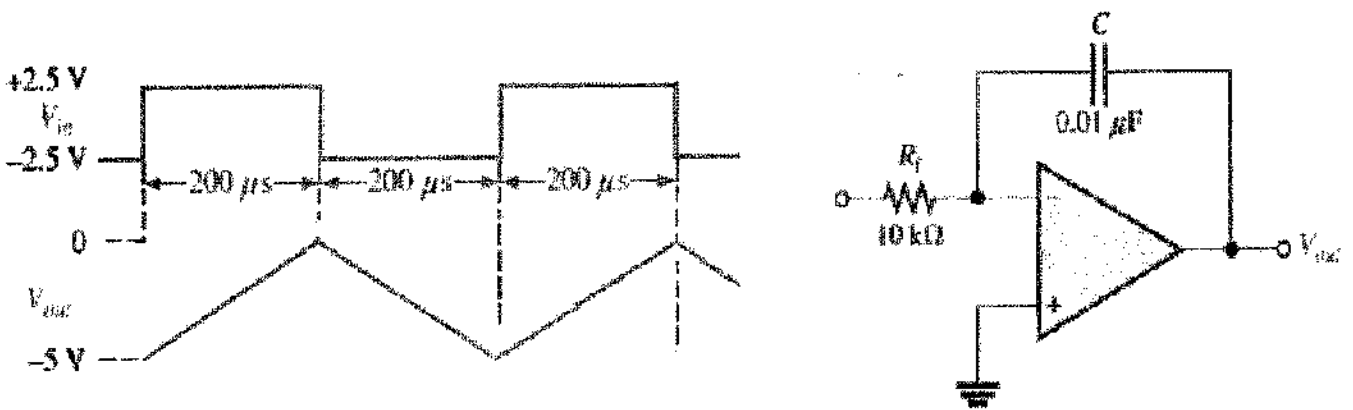5- The following waveform describes the output voltage of the ideal op-amp shown below.



6- For a given value of open-loop differential gain, a higher common-mode gain result in a lower CMRR.

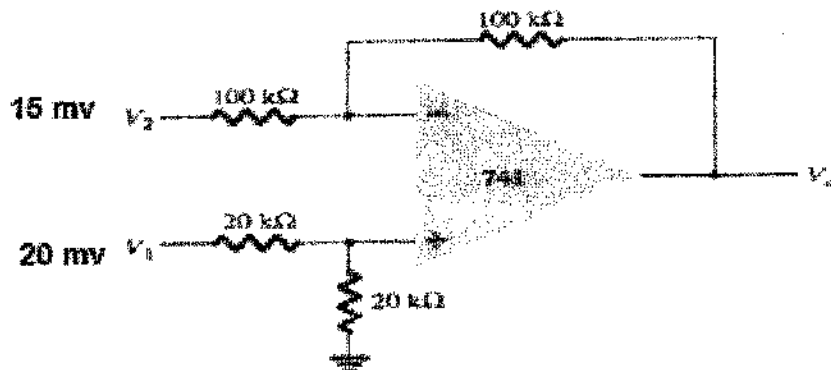7- The output voltage for the circuit shown below equal 35 mV.



8- The waveforms given in Figure (1) are observed at the indicated points in Figure (2). Assume the maximum output levels of the comparator are ± 10 .

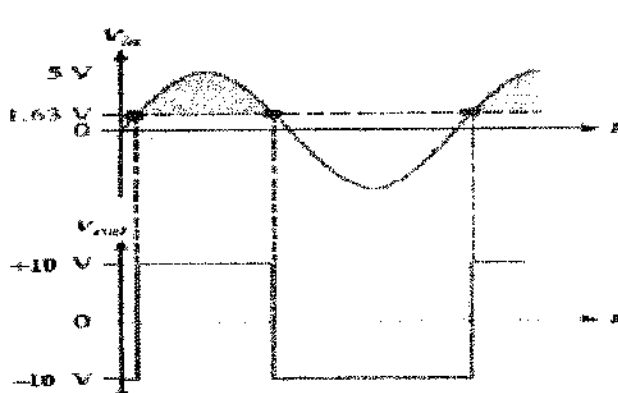


Fig. (1)

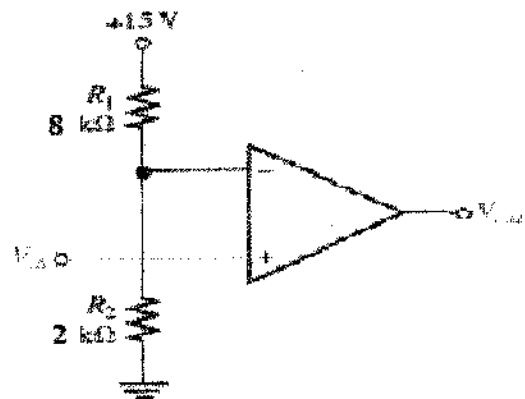


Fig. (2)

Question (2):


(30 marks)

Choose the correct answer:

1- For the Emitter Feedback Bias circuit, if the collector current tries to increase, the base voltage

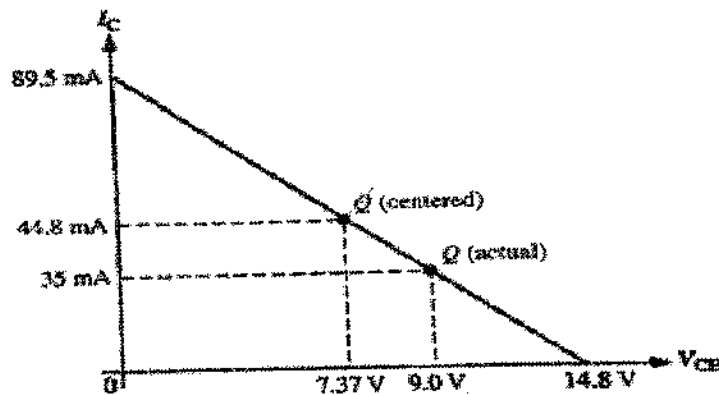
- (a) Increase (b) Decrease (c) Not affected

2- The ac load line for a specific circuit is shown below, the actual Q point for this amplifier is closer to....., therefore the maximum output current swing equal



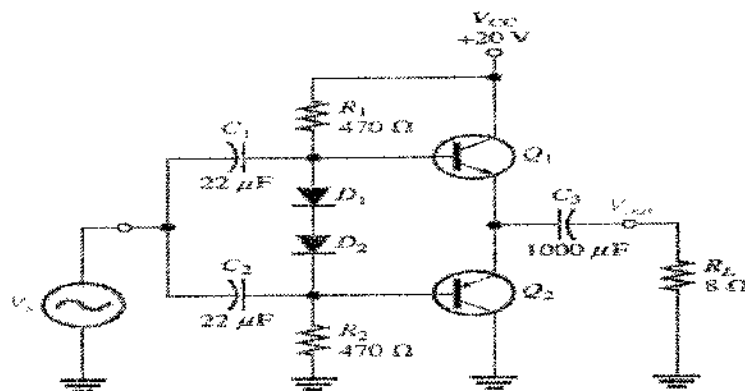- (a) Saturation, 35mA (b) Cutoff , 35mA (c) Cutoff , 9.8 mA

3- The maximum ac output power of the amplifier shown below equal



- (a) 12.5 W (b) 7.96 W (c) 6.25 W

4- The output voltage of an op-amp is 45.8 mV for input voltages of $V_{i1} = 150 \mu\text{V}$ and $V_{i2} = 140 \mu\text{V}$. The amplifier has a differential gain of $A_d = 4000$, the value of CMRR is.....

- a) 1000 b) 100 c) 105

5- There are three types of power amplifiers, the greatest efficiency is in

- a) Class A b) Class B c) Class C

6- The closed-loop critical frequency $f_{c(cl)}$ of an op-amp is its open loop critical frequency $f_{c(ol)}$.

- a) higher than b) smaller than c) equal

7- The maximum rate of change of the output voltage in response to a input voltage is defined as the slew rate of an op-amp.

- a) Step b) Square c) Ramp

8- When the open-loop gain of an op-amp is reduced by negative feedback, the bandwidth is

- a) Increased b) Decreased c) not affected

9- A certain op-amp has three internal amplifier stages with midrange gains of 40 dB, 32 dB, and 20 dB. Each stage also has a critical frequency associated with it as follows: $f_{c1} = 2$ kHz, $f_{c2} = 40$ kHz, and $f_{c3} = 150$ kHz. The total phase shift through the amplifier is, when the signal frequency is 2 kHz.

- a) -40.8° b) -48.6° c) -43°

10- is a circuit that produces aperiodic waveform on its output with only the dc supply voltage as an input.

- a) Oscillator b) Voltage amplifier c) Power amplifier

Best wishes

Dr. Amira El Attar