



This exam measures ILOs no: a3, a4,a5,a8 ,a14, b6,c7

[1] Question One [20 degrees]:

1. Explain the structure and the principle of operation of enhancement MOSFET. Why use the V- MOSFET [5 degrees]?
2. For the fixed-bias configuration of Fig. 1, determine: [8 degrees]
 - (a) I_{DQ} and V_{GSQ} using a purely mathematical approach.
 - (b) Repeat part (a) using a graphical approach and compare results.
 - (c) Find V_{DS} , V_D , V_G , and V_S using the results of part (a)
3. Sketch the basic structure of n- channel JFET. [2 degrees]
4. For the network in Fig.2. The maximum power dissipation $P_{Dmax}=800mw$, $V_{CEm}=15v$, $I_{cm}=100ma$. Find: $V_{cem}=?$ Without exceeding rating. [5 degrees]

[2] Question Two[25]:

1. Sketch the r-parameter transistor models, and the relation of transistor symbol to r-parameter model. [5 degrees]
2. Sketch the load line for BJT in all its possible cases? [4 degrees]
3. Prove the relation between β and α then prove that $I_{CE0}= I_{CB0} (1+\beta)$. [5degrees]
4. explain the effect of swamping on the amplifier input resistance? [3 degrees]
5. Determine the following for the network in Fig.3. (a) $S(I_{CO})$. (b) $S(V_{BE})$.
 - (c) $S(\beta)$ using T_1 as the temperature at which the parameter values are specified and $\beta (T_2)$ as 25% more than $\beta (T_1)$.
 - (d) Determine the net change in I_C if a change in operating conditions results in I_{CO} increasing from 0.2 to 10 μA , V_{BE} drops from 0.7 to 0.5 V, and β increases 25%. [8 degrees]

6. Find the overall maximum voltage gain for the amplifier in Figure 4 with $1\text{ k}\Omega$ a load if it is being driven by a $300\text{ k}\Omega$ source. [6 degrees]

