



This Exam measures the ILOs [a.1, a.5, b.5, b.14, c.5, and c.13]

Answer the following questions: In each question, draw the circuit diagram and necessary phasor diagrams and write the necessary equations to clarify your answer

Question One: (15 Mark) [measures the ILOs of a1.2, a.5.1, b.5., c.13.2, and c.13.4]

- Show**, experimentally, how voltage regulation and transmission efficiency can be determined for medium lines using *T*- method.
- Explain** the relation between the receiving end power factor and the performance of transmission lines.
- Illustrate** the expected relation between sending end voltage and receiving end voltage at lightly and no load conditions of medium transmission lines

Question (2): (15 Mark) [measures the ILOs of a1.2, , b.5, and c.13.4]

- Define** the voltage regulation. Under what load condition(s), a positive voltage regulation may be obtained? **Verify** your answer by the aid of phasor diagrams for a single-phase transformer.
- Discuss** two methods used to improve the poor voltage regulation.
- A 15 KVA, 2400/240 V single-phase transformer has the following test results:

Test	Voltage (V)	Current (A)	Power (W)
Open-circuit	240	2.3	60
Short circuit	49	6.25	150

- Illustrate** the side at which the measuring instruments were located for both tests, **according** to the given table.
- Estimate** the transformer equivalent circuit parameters referred to low voltage -side
- Determine** the efficiency and voltage regulation if the transformer is operating at **80% full load** and a power factor of 0.9 lagging.

Question (3): (15 Mark) [measures the ILOs of a.5.3, b.14.1, and c.13.4]

- Define** the power factor. **What** are the measurements in the laboratory that necessary to get the power factor?

- b) Draw the connection diagram to perform the power factor improvement identifying the reading of each meter and hence write the necessary equation to find the required KVAR for:-
- Lagging power factor.
 - Leading power factor.
- c) A single- phase motor connected to a power supply at 380 V takes 33 A at 0.7 power factor lagging. It is desired to improve the power factor of the receiving end to 0.92 lagging value. Calculate the capacitance required in parallel with the motor to reach this value.
-
-

Question (4): (15 Mark) [a.1.2, b.5, and c.13.4]

- a) Explain the difference between the auto-transformer and the conventional transformer.
- b) Discuss what will happen in each of the following practical case:
- the magnetic core of a transformer is replaced by non-magnetic core
 - A 380 Volts 50 Hz supply is connected to the primary of a transformer rated at 50 Hz, 230/115 V
 - Short-circuit test of a transformer is performed under 80 % of rated voltage
 - The load of a medium transmission line is reduced to 20% of full load.
 - The bundled transmission lines is used at high voltage level
 - One phase of the secondary winding of a Δ - Δ three-phase transformer is open

Best wishes

Committee of corrections and Testers

