




This exam measures ILOs no: 1, 4, a, 8, a, 13, a, 14, a, 15, a, 2, b, 5, b, 16, c, 18, c, 17, d, 7

[1] Question One [25 degrees]:

1- In figure 1. The regulator has load current varies from 0-1A and the unregulated d.c. input varies from 12-18v. the 8.5v zener diode requires at least 1 mA of current to stay in its regulation region ($I_{Z(min)}=1\text{mA}$). [15 degrees]

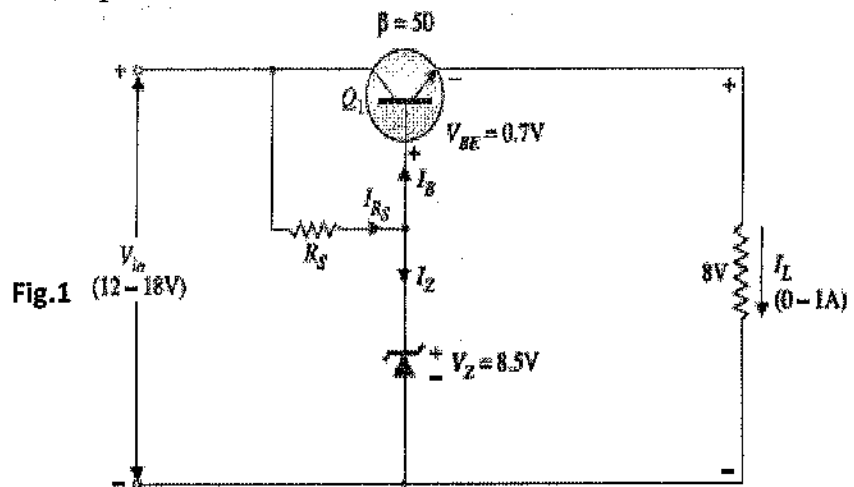- a- what is the type of this regulator, explain its principle of operation.
- b- determine the value of R_s to ensure proper circuit operation.
- c- determine maximum power dissipation in R_s .
- d- determine maximum power dissipation in zener diode.



2- Design regulator circuit suitable for high current application with explanation. [100 degrees]

[2] Question Two [30 degrees]:

1. write short note about the following with a neat diagram : [15 degrees]

- a- R_C phase shift oscillators and get an expression of its resonance frequency when $R = R_L$.
- b- crystal oscillators and get an expression of its resonance frequency.



2. A Wien Bridge Oscillator circuit is required to generate a sinusoidal waveform of 5200 Hertz (5.2kHz). Calculate the values of the frequency determining resistors R_1 and R_2 and the two capacitors C_1 and C_2 to produce the required frequency. If the oscillator circuit is based around a non-inverting operational amplifier configuration, determine the minimum values for the gain resistors to produce the required oscillations. Finally draw the resulting oscillator circuit [12 degrees]

[3] Question Three [20 degrees]:

1. Sketch the block diagram of transistor Astable Multivibrator and explain its operation. Sketch the output signal varying with time. [10 degrees]
2. Design Hartley oscillator circuit has operating frequency of $f = 2.989 \text{ kHz}$. [10 degrees]

[4] Question Four [25 degrees]:

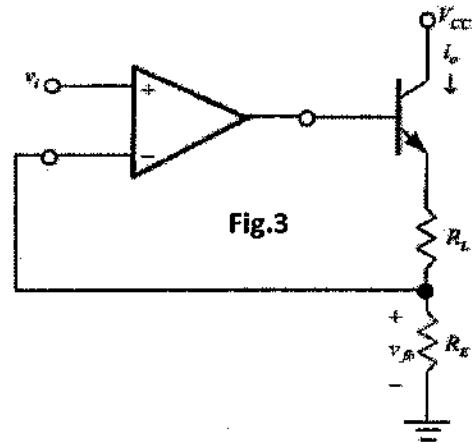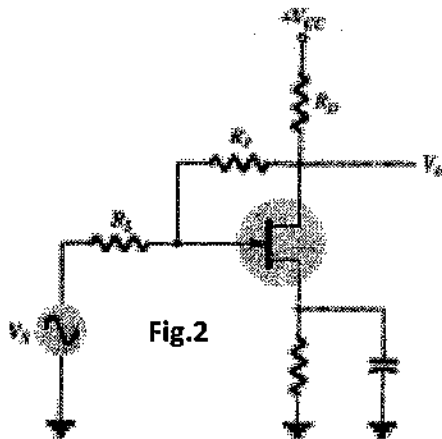1. Find the equivalent circuit of Fig. 2, then calculate the voltage gain with and without feedback. With values of $g_m = 5 \text{ mS}$, $R_D = 5.1 \text{ k}$, $R_S = 1 \text{ k}$, and $R_F = 20 \text{ k}$. [12 degrees]
2. Figure 3. Presents an OP-AMP followed by a BJT common collector amplifier, the resistance R_E provides the negative feedback. Given $R_i = 50 \text{ k}\Omega$, $A_v = 1000$, $R_o = 100 \Omega$, $I_C = 2 \text{ mA}$, $h_{FE} = 100$. Further, $R_E = 100 \Omega$, $R_L = 1 \text{ k}\Omega$. Find the ac equivalent circuit of the connected system. Then calculate the gain i_o/v_i , R_{if} , and R_{of} . [13 degrees]



[*] Question [7 degrees]:

Write about one of the following:

1. Dielectric resonator oscillator.
2. Nano technology.
3. Automatic gain control.
4. Power amplifier classifications.